

1. (a) (i)  $E = (Pt) = 36 \times 3600$   
*allow*  $I = 3 \text{ A}$  and  $E = VIt$ , etc. **C1**
- $= 1.3 \times 10^5 \text{ (J)}$   
*accept*  $129600 \text{ (J)}$  **A1**
- (ii)  $Q = E/V = 1.3 \times 10^5/12$  or  $Q = It = 3 \times 3600$   
*ecf (a)(i)* **C1**
- $= 1.1 \times 10^4$   
*accept*  $1.08 \times 10^4$  **A1**
- unit: C  
*allow*  $\text{A s}$  *not*  $\text{J V}^{-1}$  **B1**
- (iii)  $Q/e = 1.1 \times 10^4/1.6 \times 10^{-19}$   
*ecf (a)(ii)* **C1**
- $= 6.9 \times 10^{22}$   
*accept*  $6.75$  or  $6.8 \times 10^{22}$  *using*  $10800$  **A1**
- (b) (i) *no mark for quoting formula*
- the average displacement/distance travelled of the electrons along the wire per second;  
*allow* *in one second* **B1**
- (over time/on average) they move slowly in one direction through the metal/Cu lattice (when there is a p.d. across the wire); **B1**
- (because) they collide constantly/in a short distance with the lattice/AW  
*max 2 marks from 3 marking points* **B1**

- (ii) select
- $I = nAev$
- (= 3.0 A)

*1 mark for correct formula*

C1

$$v = 3.0/8.0 \times 10^{28} \times 1.1 \times 10^{-7} \times 1.6 \times 10^{-19}$$

*1 mark for correct substitutions into formula*

C1

$$= 2.1 \times 10^{-3} \text{ (m s}^{-1}\text{)}$$

*1 mark for correct answer to 2 or more SF*

A1

[12]

2. (a) (i) Electrons in a metal  
(ii) Ion in an electrolyte

B1

B1

- (b) 1.  $I = Q/t / I = 650/5$   
 $I = 130 \text{ (A)}$

C1

A1

2.  $n = I/e = 130/1.6 \times 10^{-19}$   
 $n = 8.1 \times 10^{20}$

C1

A1

[6]

3. (a)  $R = R_1 + R_2 / R = 200 + 120 / R = 320$

C1

$$\text{current} = \frac{8.0}{320}$$

C1

$$\text{current} = 2.5 \times 10^{-2} \text{ (A)}$$

A0

- (b)  $V = 25 \times 10^{-3} \times 120 / V = \frac{120}{120 + 200} \times 8.0$   
 $V = 3.0 \text{ (V)}$  (Possible ecf)

B1

- (c) p.d. across the 360 ( $\Omega$ ) resistor = p.d. across the 120 ( $\Omega$ ) resistor /  
There is no current between **A** and **B** / in the voltmeter  
(Allow 'A & B have same voltage' - BOD)

B1

The p.d. calculated across 360  $\Omega$  resistor is shown to be 3.0 V /  
The ratio of the resistances of the resistors is shown to be the same.

B1

[5]

4. (a) Into the page

B1

- (b)  $I = \frac{\Delta Q}{\Delta t}$  (Allow other subject, with or without  $\Delta$ )

C1

(charge =)  $7800 \times 0.23$  C1  
 $1.794 \times 10^3 \approx 1.8 \times 10^3$  (C) (Ignore minus sign) A1  
 $(1.8 \times 10^6$  (C) scores 2/3)

(c) (number =)  $\frac{1.79 \times 10^3}{e}$  (Possible ecf) C1  
(number =)  $1.12 \times 10^{22} \approx 1.1 \times 10^{22}$  A1

**[6]**

5. (a)  $Q = It$  (Allow any subject) C1  
 $Q = 0.040 \times 5.0 \times 60 \times 60 \setminus$   $Q = 0.040 \times 1.8 \times 10^4$   
charge = 720 A1  
 $(40 \times 5 = 200$  or  $0.040 \times 5 = 0.02$  or  $40 \times 1.8 \times 10^4 = 7.2 \times 10^5$  scores 1/2)  
coulomb \ C \ As B1

(b) It is less because the average current is less \ area (under graph) is less \  
current 'drops' after 3 hours. B1

**[4]**

6. (a) Ammeter in series B1  
Voltmeter in parallel (across the ends of the wire) B1

- (b)  $\rho = \frac{RA}{L}$  (Allow any subject) M1
- $R$  = resistance,  $L$  = length and  $A$  = (cross-sectional) area A1  
 ( $\rho$  = resistivity is given in the question)
- Any **four** from:
- Measure the length of the wire using a ruler B1
- Measure the diameter of the wire B1  
 using a micrometer \ vernier (calliper) B1
- Calculate the (cross-sectional) area using  $A = \pi r^2$  \  $A = \pi d^2/4$  B1
- Calculate the resistance (of the wire) using  $R = \frac{V}{I}$  B1
- Repeat experiment for different lengths \ current \ voltage \ diameter  
 (to get an average) B1
- Plot a graph of  $R$  against  $L$ . The gradient =  $\rho/A$ . B1  
 (Or Plot  $V$  against  $I$ . The gradient is  $\rho L/A$ )
- Structure and organisation. B1
- Spelling and grammar. B1

[10]

**QWC**

The answer must involve physics, which attempts to answer the question.

**Structure and organisation**

Award this mark if the whole answer is well structured.

**Spelling and Grammar mark**

More than two spelling mistakes or more than two grammatical errors means the SPAG mark is lost.

7. Coulomb / C B1

[1]

8. (a) Parallel B1
- (b) (i)  $I = \frac{12}{8.0}$  C1  
 current = 1.5 (A) A1
- (ii)  $P = \frac{V^2}{R}$  /  $P = IV$   $P = I^2 R$  C1  
 $P = \frac{12^2}{8}$  /  $P = 1.5 \times 12$   $P = 1.5^2 \times 8.0$  (Possible ecf) C1  
 power = 18 (W) A1
- (iii)  $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \left(\frac{1}{R_3}\right)$  /  $\frac{1}{R} = \frac{1}{8} + \frac{1}{8} + \frac{1}{8}$  C1  
 $\frac{1}{R} = 3 \times \frac{1}{8}$  C1  
 resistance =  $2.67 \approx 2.7$  ( $\Omega$ ) (Allow answer expressed as  $8/3$ ) A1  
 (0.375 or  $3/8$  scores 2/3)
- (iv) energy =  $0.018 \times 12 \times 3$  C1  
 energy =  $0.648 \approx 0.65$  (kW h) (Possible ecf) A1  
 (0.22 (kW h) scores 1/2)  
 (648 (kW h) scores 1/2)  
 ( $2.3 \times 10^6$  (J) scores 1/2)
- (c) It will be brighter B1  
 The current is larger / correct reference to:  $P \propto 1/R$  B1

[13]

9. The sum of the currents entering a point / junction is equal to the sum of the currents leaving (the same point) Or 'Algebraic sum of currents at a point = 0' B2  
 (-1 for the omission of 'sum' and -1 for omission of 'point' / 'junction')  
 (Do not allow  $I_1 + I_2 = I_3 + I_4$  unless fully explained)

[2]