

## Definitions and Concepts for Edexcel Physics GCSE

### Topic 10: Electricity and Circuits

---

*Definitions in **bold** are for higher tier only*

*Definitions marked by '\*' are for separate sciences only*

**Alternating Current:** Current flow consisting of charges that continually change direction. These oscillations usually occur at a set frequency.

**Ammeter:** A device connected in series with a component to measure the current that flows through it.

**Amperes (Amps):** The unit of current.

**Circuit Breaker:** A safety device that cuts off the power supply if a surge of current passes through it. Circuit breakers can be reset and are quicker acting than fuses.

**Coulomb:** The unit of charge.

**Currents at a Junction:** The sum of the currents entering a junction must always equal the sum of the currents leaving it. This is a consequence of the conservation of charge.

**Diode:** A component that only allows current to flow through in the forward direction. They have very large resistances in the reverse direction.

**Direct Current:** Current flow consisting of charges flowing in a single direction only. Batteries and cells provide direct current.

**Earth Wire:** The green and yellow striped safety wire connected to metal casings, that prevents an appliance from becoming live.

**Electric Current:** The rate of flow of electrical charge. Its value is the same at any position in a single closed loop. In metals, the charges that flow are electrons.

**Energy Transfers in Circuits:** Electrical energy is transferred to thermal energy when current does work against a resistance. In metals this is a result of collisions between electrons and ions.

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)



**Filament Lamp:** A light emitting component consisting of an enclosed metal filament. Its resistance increases as the filament's temperature increases.

**Fuse:** A safety device consisting of a thin metal filament that melts and cuts off the power supply if there is a surge in current. Fuses are connected to the live wire.

**Light Dependent Resistor (LDR):** A light sensitive component whose resistance decreases as its temperature increases.

**Light Emitting Diode:** A device that gives out light when a current flows through it. Current can only flow through it in one direction, and a minimum voltage must be applied across it before it illuminates.

**Live Wire:** The brown coloured wire that carries the alternating current from the supply in a mains power supply.

**Mains Electricity:** An a.c supply, which in the UK has a frequency of 50Hz a value of 230V.

**Neutral Wire:** The blue coloured wire that completes the circuit in a mains power supply.

**Ohmic Conductor:** A conductor whose current flow is directly proportional to the potential difference across it, when held at a constant temperature.

**Ohms:** The unit of resistance.

**Ohm's Law:** The current flowing through an Ohmic conductor at constant temperature is directly proportional to the potential difference across it.

**Parallel:** Components connected in parallel have the same potential difference across each component. The total current is equal to the sum of the currents flowing through each component.

**Potential Difference:** The energy that is transferred per unit charge between two points in a circuit. It is often also called a voltage.

**Power:** The rate at which an appliance transfers energy. For a circuit component, it is equal to the product of the current passing through it and the potential difference across it.

**Resistance:** A measure of the opposition to current flow.

**Resistors in Parallel:** The total resistance is less than the lowest individual resistance.



**Resistors in Series:** The total resistance is equal to the sum of the resistances of the individual resistors.

**Series:** Components connected in series have the same current passing through each component but share the total potential difference of the power supply.

**Thermistor:** A temperature dependent component, whose resistance increases as its temperature decreases.

**Volt:** The unit of potential difference. One volt is equal to one joule per coulomb.

**Voltmeter:** A device that is connected in parallel with a component to measure the potential difference across it.

**Watt:** The unit of power.

