

Edexcel GCSE Physics

Topic 10: Electricity and circuits

Notes


(Content in bold is for Higher Tier only)

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)




The Structure of the Atom

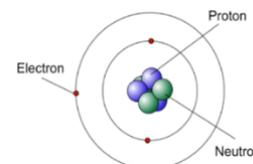Positively charged nucleus surrounded by negatively charged electrons





Subatomic Particle	Relative Mass	Relative Charge
Proton	1	+1
Neutron	1	0
Electron	0 (0.0005)	-1

Electricity

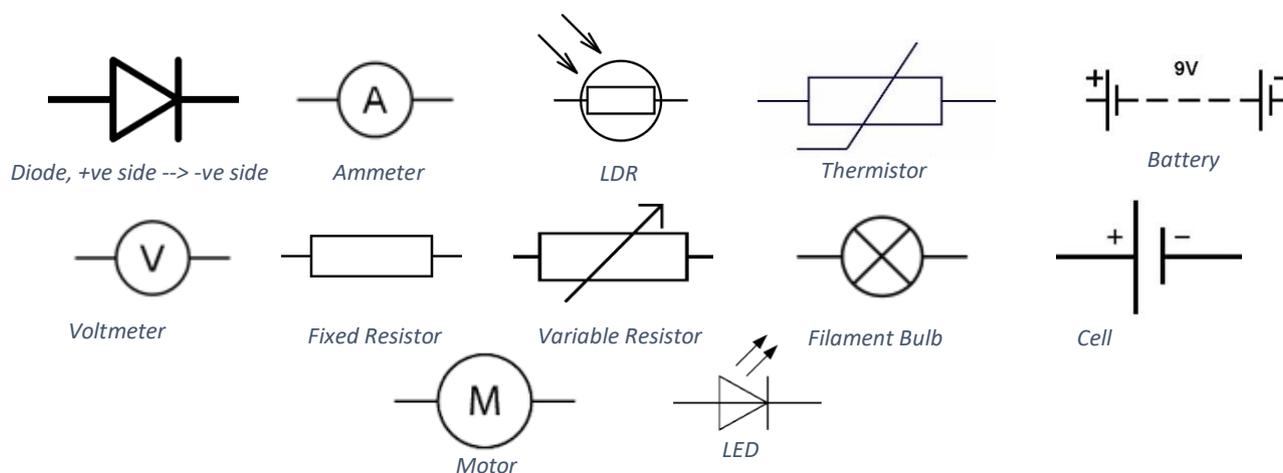

Series and Parallel

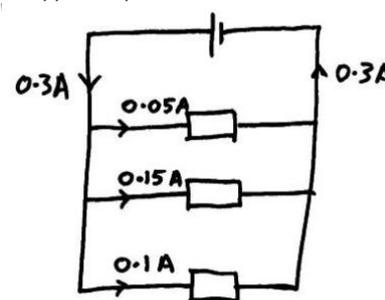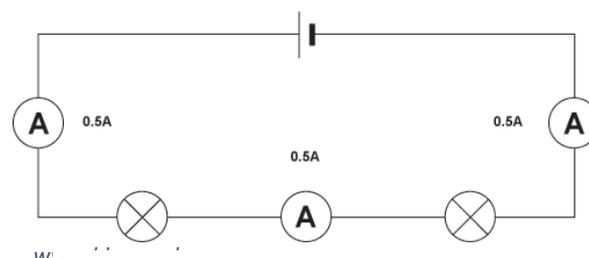- Series Circuits
 - o Closed circuit
 - o The current is the **same everywhere**
- Parallel Circuits
 - o Branched circuit
 - o Current splits into **multiple paths**
 - o **Total current into a junction = total current in each of the branches**
 - o **Voltage is the same across each "branch"**



physicsnet.co.uk

Here the resistors are not all the same hence different amounts of current flow through each branch

Potential Difference represented by 'V'

- Potential difference is measured in Volts
- Energy transferred per unit charge, Joule per Coulomb
 - o Measured across two points, as it is the amount of energy per unit charge to move from one point to the next
- Measured with a voltmeter, placed in parallel across a component
- There can be a voltage across a component, in a closed or open circuit
- When it is in a closed circuit, and there is a potential difference (voltage), current will always flow

$$E = QV$$

Energy transferred (joule, J) = charge moved (coulomb, C) × potential difference (volt, V)



Current, represented by 'I'

- Current is measured in amps
- Rate of flow of charge (the flow of electrons in the wires)
 - o Measured at any single point on the circuit
- Measured with ammeter which is placed in series
 - $V = IR$
- Potential difference (volt, V) = current (ampere, A) × resistance (ohm, Ω)

Resistance

- Greater resistance, the harder it is for charge to flow through the component, therefore the current is smaller
- Variable resistor changes the amount of resistance of the component, changing the amount of current that flows in the circuit

Series


- o Components are connected end to end
- o All the current flows through all the components
- o Can only switch them all off at once
 - PD (potential difference) is **shared** across the whole circuit
 - PD of power supply = sum of PD across each component
 - Current is the **same** through all parts of the circuit
 - Current at one point = current at any other point
 - Total Resistance is the **sum** of the resistance in each component $R_1 + R_2 = R$
 - Resistance of two components is bigger than just one of them, because the charge has to push through both of them when flowing round the circuit

Parallel

- o Components are connected separately to the power supply
- o Current flows through each one separately
- o You can switch each component off individually
 - PD is the same across all **branches**
 - PD of power supply = PD of each branch
 - Because charge can only pass through any one branch
 - Current is shared between **each** of the branches
 - Current through source = sum of current through each branch
 - Total resistance is **less** than the branch with the smallest resistance
 - Two resistors in parallel will have a smaller overall resistance than just one – $1/R_1 + 1/R_2 = 1/R$
 - Because charge has more than one branch to take, so only some charge will flow along each branch



Device Characteristics

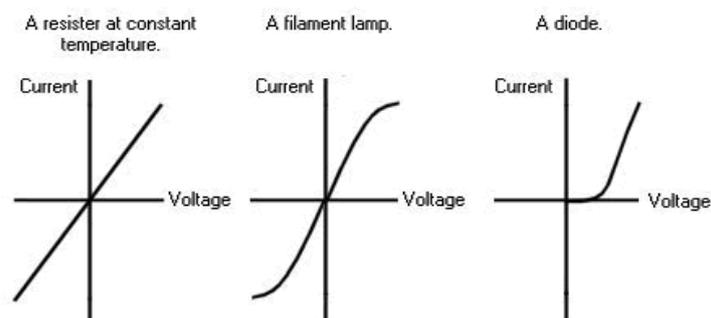

inteleducationresources.intel.co.uk – gradient of each is $1/\text{resistance}$, so a sharper gradient means a lower resistance

How resistance changes

- With current
 - As current increases, electrons (charge) has **more energy**
 - When electrons flow through a resistor, they collide with the ions in the resistor
 - The current here is doing work against the resistance
 - This transfers energy to the **ions**, causing them to **vibrate more (heating resistor)**
 - This makes it more **difficult** for electrons to flow through the resistor
 - So resistance increases, and current decreases
 - This may be a benefit, as some appliances like a toaster use heating filaments that have a high resistance to get hot easily.
- With temperature
 - Normal wires - See above, the same process occurs as atoms vibrate when hot
 - THERMISTOR ONLY
 - Hotter temperatures, resistance is lower
 - Used in temperature detectors/thermostats
- With Length
 - Greater length, the more resistance, and the lower the current
 - Electrons make their way through more resistor atoms, so it is harder to get through than if you were using a shorter wire
- With Cross Sectional Area
 - Thinner wires give greater resistance
 - Because less overall room for electrons to pass through between atoms
- With Light
 - LDR (Light Dependent Resistor) ONLY
 - Greater the intensity of light, the lower the resistance
 - So resistance greatest when dark
 - Used in automatic night lights
- With Voltage
 - DIODE ONLY
 - Diode allows current to flow freely in one direction
 - In the opposite direction, it has a very high resistance, so no current can flow

Efficiency – low resistance wires means less energy loss as current flows through the circuit



Testing Relationships:

- Points for All
 - Make sure component(s) **do not overheat**, leave to cooldown between each reading
 - **Repeats and take average**
- Varied wire resistance
 - Wires ranging in resistance from 1Ω to 10Ω
 - Connected to DC of 2, 4, 6, ..., 10, 12V
 - Connected in series to an Ammeter, parallel to Voltmeter
 - Make sure all the other wires used have **negligible resistance**
 - Measure the current for each voltage for each wire
 - **Plot a graph** to show the relationship between the pd and current
- Filament Lamps
 - Connected to DC of 2, 4, 6, ..., 10, 12V
 - Connect the filament lamp to Ammeter in series and Voltmeter in parallel,
 - Measure the current for each voltage
 - **Plot a graph** to show relationship between the pd and current
 - Non-linear shows R varies
- Diodes
 - Connected to DC of 1, 1.5, 2, 4, 6, ..., 10, 12V
 - Connect to an Ammeter in series and Voltmeter in parallel,
 - Measure the current for each voltage
 - Switch the diode the other way round to record current for -1, -1.5, -2, -4V
 - **Plot graph for the positive and negative potential differences** to show the relationship
- LDR
 - Constant voltage of 12V
 - Connect to ammeter
 - Shine lamp immediately onto LDR and measure current
 - Move the lamp $\sim 10\text{cm}$ away and measure current
 - Keep doing this until 50cm
 - Calculate resistance at each light intensity
 - **Plot graph** of resistance against light intensity
- Thermistor
 - Constant voltage of 12V
 - Connect to an Ammeter
 - Place in ice water with thermometer
 - Measure current at 0 degrees.
 - Add hot water and stir, measuring current at 10, 20, ..., 60 degrees
 - Calculate the resistance
 - **Plot a graph** of resistance against temperature



Power

- Energy transferred (joule, J) = current (ampere, A) × potential difference (volt, V) × time (second, s)

$$E = I V t$$

- Power is energy transferred per second $P = \frac{E}{t}$
- Power is directly proportional to current and voltage, so doubling current doubles power

$$P = IV$$
- Electrical power (watt, W) = current (ampere, A) × potential difference (volt, V)

$$P = I^2 R$$
- Electrical power (watt, W) = current squared (ampere², A²) × resistance (ohm, Ω)
- Power loss is proportional to resistance, and to current squared
- Energy is transferred from **chemical potential in batteries to electrical energy** in wires to any form of useful energy in the devices they power

AC/DC

- AC is alternating current, which comes from the mains
 - o Current continuously varies, from positive to negative (charge changes direction)
- DC, direct current, is the movement of charge in one direction only
 - o Cells and batteries supply direct current
- In the UK, mains supply is at 50Hz and 230V

Plug

- In a plug there are 3 different wires
- Live wire
 - o This is a brown colour
 - o It carries voltage from mains to appliance
 - o This may be dangerous even if mains circuit is off, as current may still be flowing through it
- Neutral Wire
 - o This is a blue colour
 - o Completes the circuit
- Earth wire
 - o This has green and yellow stripes
 - o **It is the safety wire used to stop the appliance becoming live**
 - o It is connected to the earth and to the casing
 - o If the live wire touches the metal casing of the appliance, it will become live (you'll get a serious electric shock if you touch it, as current flows through you to the ground)
 - o The earth wire is connected to the metal casing, and its low resistance means the current will go from the casing through the earth wire and to the ground
- Fuse
 - o **Connected to the live wire**
 - o If a large current passes through live wire, fuse heats up and melts, breaking the circuit – **preventing a fire** or damage

Power Rating – the power of the appliance when in use

- Greater power rating, greater energy consumption per second
 - o So uses more energy in a given time

