

# WJEC (Eduqas) Physics GCSE

## 7.2: Series and Parallel Circuits

### Detailed Notes

(Content in **bold** is for higher tier **only**)

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)






## Types of Circuit
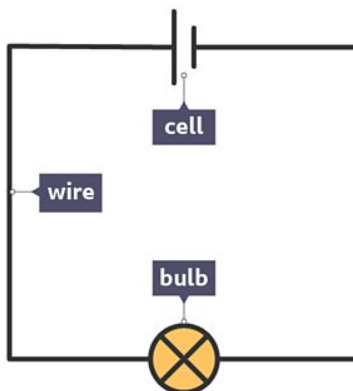
### Series


A series circuit is a **closed** electrical system with a **single path** for current to flow. This current is the **same everywhere** in the circuit and the **sum of p.d.s** is equal to the supply voltage.



*A simple series circuit (bbc.co.uk)*
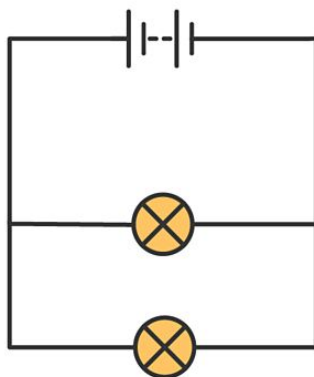
### Parallel

A parallel circuit is a **branched** electrical system with **multiple paths** (branches) for current to flow. The total current at a circuit junction equals the **sum of current** along each of the branches. The p.d. across each branch is the **same**.



*A simple parallel circuit (bbc.co.uk)*

## Calculating Resistance

Total resistance in a circuit varies depending on whether the components are connected in series or parallel.



## Series

Adding components in **series increases** the total resistance as it is the **sum** of separate resistances:

$$R_T = R_1 + R_2 + \dots$$


## Parallel

Adding components in **parallel reduces** the total resistance in a circuit. **This total resistance can also be calculated as the sum of the reciprocals** of each component resistance:

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$
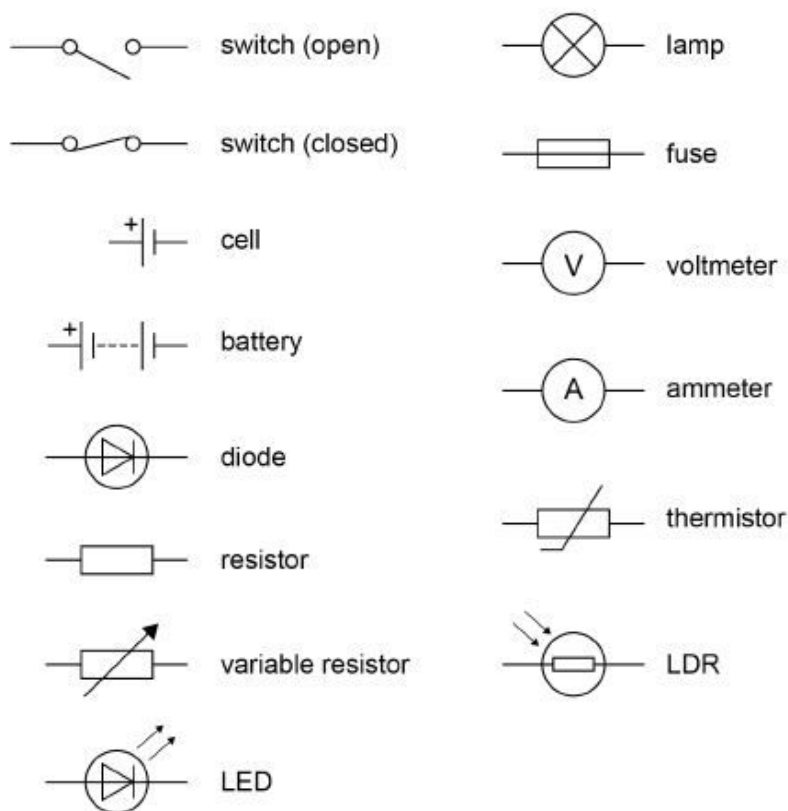
## Circuit Symbols

Symbols are used to represent the different **components** of electrical circuits.



*Common electrical circuit symbols (studyrocket.co.uk)*

