

Definitions and Concepts for WJEC (Wales) Physics GCSE

Topic 1.1: Electric Circuits

*Definitions in **bold** are for higher tier only*

Definitions marked by '' are for separate sciences only*

Ammeter: A device connected in series with a component to measure the current that flows through it.

Amperes (Amps): The unit of current.

Currents at a Junction: The sum of the currents entering a junction must always equal the sum of the currents leaving it. This is a consequence of the conservation of charge.

Diode: A component that only allows current to flow through in the forward direction. They have very large resistances in the reverse direction.

Electric Current: The rate of flow of electrical charge. Its value is the same at any position in a single closed loop. In metals, the charges that flow are electrons.

Energy Transfers in Circuits: Electrical energy is transferred to thermal energy when current does work against a resistance. In metals this is a result of collisions between electrons and ions.

Filament Lamp: A light emitting component consisting of an enclosed metal filament. Its resistance increases as the filament's temperature increases.

Light Dependent Resistor (LDR): A light sensitive component whose resistance decreases as its temperature increases.

Light Emitting Diode: A device that gives out light when a current flows through it. Current can only flow through it in one direction, and a minimum voltage must be applied across it before it illuminates.

Ohmic Conductor: A conductor whose current flow is directly proportional to the potential difference across it, when held at a constant temperature.

Ohms: The unit of resistance.

This work by [PMT Education](https://www.pmt.education) is licensed under [CC BY-NC-ND 4.0](https://creativecommons.org/licenses/by-nc-nd/4.0/)



Ohm's Law: The current flowing through an Ohmic conductor at constant temperature is directly proportional to the potential difference across it.

Parallel: Components connected in parallel have the same potential difference across each component. The total current is equal to the sum of the currents flowing through each component.

Potential Difference: The energy that is transferred per unit charge between two points in a circuit. It is often also called a voltage.

Power: The rate at which an appliance transfers energy. For a circuit component, it is equal to the product of the current passing through it and the potential difference across it.

Resistance: A measure of the opposition to current flow.

Resistors in Parallel: The total resistance is less than the lowest individual resistance. **It is equal to the inverse of the sum of the inverses of the individual resistances.**

Resistors in Series: The total resistance is equal to the sum of the resistances of the individual resistors.

Series: Components connected in series have the same current passing through each component but share the total potential difference of the power supply.

Thermistor: A temperature dependent component, whose resistance increases as its temperature decreases.

Volt: The unit of potential difference. One volt is equal to one joule per coulomb.

Voltmeter: A device that is connected in parallel with a component to measure the potential difference across it.

Watt: The unit of power.

