

## Mark schemes

## Q1.

(a) 50 (Hz)

1

230 (V)*this order only*

1

(b) 340 mW = 0.34 W

1

$$0.34 = 0.75^2 \times R$$

*allow a correct substitution of an incorrectly / not converted value of P*

1

$$R = \frac{0.34}{0.75^2}$$

*allow a correct rearrangement of an incorrectly / not converted value of P*

1

$$R = 0.60 \text{ } (\Omega)$$

*allow an answer consistent with an incorrectly / not converted value of P**allow a correct answer given to more than 2 sf*

1

(c) the dirt changes the (measured) resistance of the coin

**or**

the (measured) resistance is different from the expected resistance (of the coin)

*allow the measured resistance does not match the resistance of a known coin**allow dirt stops charge flow (through the coin)**allow dirt stops the current (in the coin)*

1

(d)



1

(e)  $R_{Total} = 400 + 80 (= 480 \Omega)$

1

$$12 = I \times 480$$

or

$$I = \frac{12}{480}$$

*allow a correct substitution / rearrangement with  $R_{Total}$  in range 470 - 490  $\Omega$*

1

$$I = 0.025 \text{ (A)}$$

*allow a correct calculation using  $R_{Total}$  in range 470 - 490  $\Omega$*

1

$$V = 0.025 \times 80$$

*allow a correct substitution using their calculated value of  $I$  (using  $V = IR$ ) and  $R_{Th}$  in range 70 - 90  $\Omega$*

1

$$V = 2.0 \text{ (V)}$$

*allow a correct calculation using their calculated value of  $I$  (using  $V = IR$ ) and  $R_{Th}$  in range 70 - 90  $\Omega$*

**OR**

$$\text{total } R = 400 + 80 (= 480) \text{ (1)}$$

$$\text{ratio (Th:R)} = 80:480 \text{ (1)}$$

$$\text{ratio} = 1:6 \text{ (1)}$$

$$V = \frac{1}{6} \times 12 \text{ (1)}$$

$$V = 2.0 \text{ (V) (1)}$$

*allow a range of  $R_{Th}$  between 70 and 90  $\Omega$*

*allow a correct ratio using a value of  $R_{Th}$  between 70 and 90  $\Omega$*

*allow a correct substitution using a value of  $R_{Th}$  between 70 and 90  $\Omega$*

*allow an answer in the range 1.8 (V) to 2.2 (V)*

1

**[13]**

**Q2.**

(a)



1

(b)  $t = 0.400 \text{ (s)}$ 

1

$$2.0 = I \times 0.400$$

*allow a correct substitution of an incorrectly / not converted value of  $t$*

1

$$I = \frac{2.0}{0.400}$$

*allow a correct rearrangement using an incorrectly / not converted value of  $t$*

1

$$I = 5.0 \text{ (A)}$$

*allow an answer consistent with an incorrectly / not converted value of  $t$*

1

**[5]****Q3.**

(a) **Level 3:** The method would lead to the production of a valid outcome. The key steps are identified and logically sequenced.

5-6

**Level 2:** The method would not necessarily lead to a valid outcome. Most steps are identified, but the method is not fully logically sequenced.

3-4

**Level 1:** The method would not lead to a valid outcome. Some relevant steps are identified, but links are not made clear.

1-2

**No relevant content**

0

**Indicative content**

- ammeter in series with filament lamp
- current measured with an ammeter
- voltmeter in parallel with filament lamp
- p.d. measured with a voltmeter
- variable resistor (or variable power pack or variable number of cells) used to vary current in and p.d. across filament lamp
- range of p.d. of 0 to 6 V
- interval of p.d. of 1 V
- reverse connections to power supply to obtain negative values
- take repeat readings and calculate a mean
- discard anomalies

Indicative content may be seen in a circuit diagram.

Level 3 answer: needs to include a circuit which would work (if included) and a method to obtain negative values.

(b)  $3.0 = 0.16 \times R$

*allow a correct substitution of an incorrect value of  $I$  in the range 0.15 (A) to 0.17 (A)*

1

$$R = \frac{3.0}{0.16}$$

*allow a correct rearrangement of an incorrect value of  $I$  in the range 0.15 (A) to 0.17 (A)*

1

$$R = 18.75 (\Omega)$$

*allow 19 ( $\Omega$ )*

*allow 18.8*

1

(c)  $t = 1800 (\text{s})$

1

$$Q = 0.21 \times 1800$$

*all subsequent marks can score if an incorrectly / not converted value of  $t$  is used*

1

$$Q = 378 (\text{C})$$

1

$$E = 378 \times 6.0$$

1

$$E = 2268 (\text{J})$$

*allow an answer to 2 or 3 s.f.*

**OR**

$$P = 0.21 \times 6.0 \text{ (1)}$$

$$P = 1.26 \text{ (W) (1)}$$

$$t = 1800 \text{ (s) (1)}$$

*all subsequent marks can score if an incorrectly / not converted value of  $t$  is used*

$$E = 1.26 \times 1800 \text{ (1)}$$

$$E = 2268 \text{ (J) (1)}$$

*allow an answer to 2 or 3 s.f.*

1

- (d) (for the power to quadruple) the current and the p.d. would both need to double

1

(but the current doesn't double) because the resistance of the filament lamp increases

**or**

(but the current doesn't double because the graph shows that) current is not proportional to p.d.

*allow the graph does not show direct proportionality*


*ignore the graph is not a straight line*

*ignore the graph is not linear*

1

**[16]****Q4.**

(a)

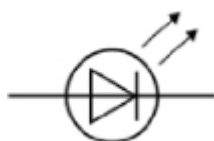

*allow:*



1

**[1]**