

Questions are for both separate science and combined science students**Q1.****Figure 1** shows a student putting a coin into a vending machine that sells food.**Figure 1**

- (a) The vending machine is connected to the mains electricity supply.

What is the frequency and the potential difference of the mains electricity supply in the UK?

Frequency = _____ Hz

Potential difference = _____ V

(2)

The vending machine identifies the value of the coin by measuring the resistance of the coin.

- (b) The power dissipated by the coin is 340 mW when the current in the coin is 0.75 A.

Calculate the resistance of the coin.

Use the Physics Equations Sheet.

Resistance = _____ Ω

(4)


- (c) Coins that are dirty are **not** recognised by the vending machine.

Suggest **one** reason why.

(1)


Figure 2 shows part of a different circuit that is used to monitor the temperature inside the vending machine.

Figure 2

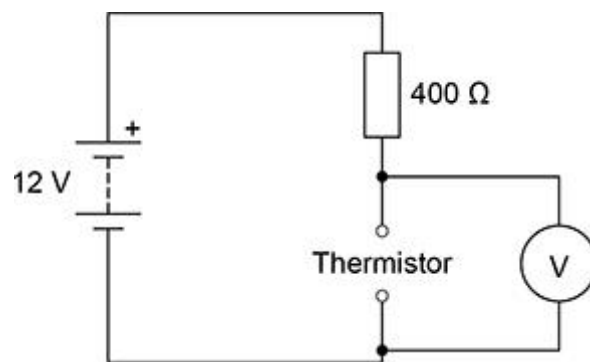

 - (d) The circuit symbol for a thermistor has not been included.


Draw the circuit symbol for a thermistor in the box below.



(1)

Figure 3 shows how the resistance of the thermistor varies with temperature.

Figure 3

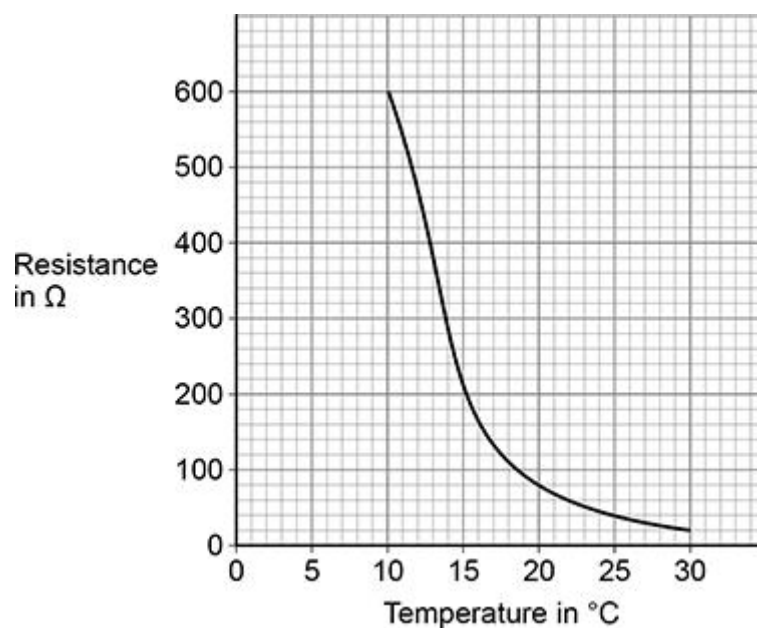

- (e) The cooling system inside the vending machine turns on when the temperature of the thermistor is above 20°C .

Determine the potential difference across the thermistor when the temperature is 20°C .

Use the Physics Equations Sheet.

Potential difference = _____ V

(5)


(Total 13 marks)

Q2.


The live wire in a three-core cable is connected to a fuse inside a plug.

A fuse contains a wire that is designed to melt when the current gets too great.

The figure below shows a fuse.

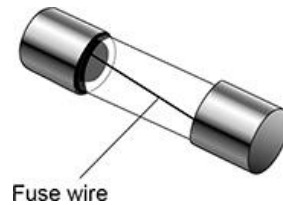

 - (a) Draw the circuit symbol for a fuse in the box below.



(1)

- (b) The fuse wire melts when there is a charge flow of 2.0 C for 400 ms.

Calculate the current in the fuse wire.

Use the Physics Equations Sheet.

Current = _____ A


(4)

(Total 5 marks)

Q3.

A student investigated how the current in a filament lamp varies with the potential difference across the filament lamp.

The figure below shows the results.

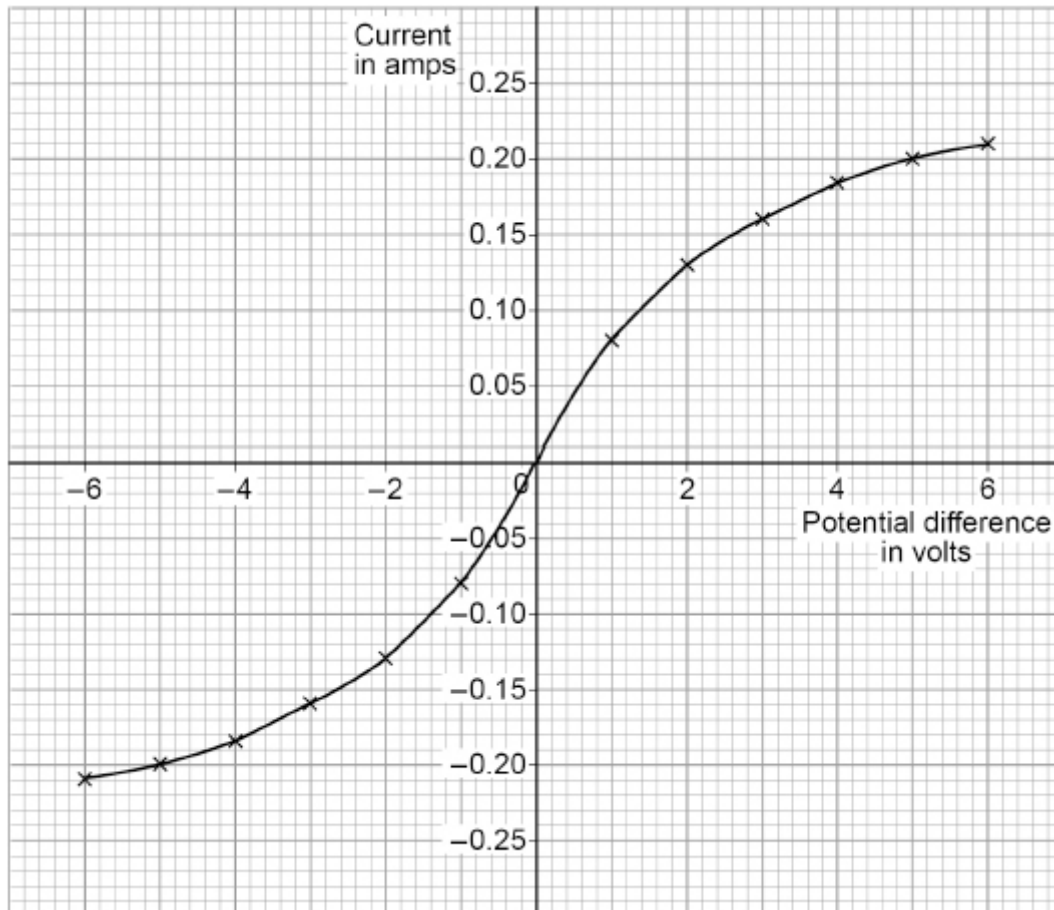

(a) Describe a method the student could use to obtain these results.

You should include a circuit diagram.

(6)

- (b) Determine the resistance of the filament lamp when the potential difference across it is +3.0 V.

Use the Physics Equations Sheet.

Use the figure above.

Resistance = _____ Ω

(3)

- (c) The current in the lamp is 0.21 A when the potential difference across the lamp is 6.0 V.

Calculate the energy transferred by the filament lamp in 30 minutes.

Use the Physics Equations Sheet.

Energy transferred = _____ J

(5)

- (d) The power output of the lamp is 1.0 W when the potential difference across the lamp is 5.0 V.

A student predicts that the power output would be 4.0 W if the potential difference was doubled.

Explain why the student is **not** correct.

(2)

(Total 16 marks)


Q4.**Figure 1** shows some hair straighteners.

Hair straighteners contain heating elements.

Figure 1

- (a) When the hair straighteners reach normal operating temperature, an LED turns on.

Draw the circuit symbol for an LED in the box.

 **(1)****(Total 1 marks)**