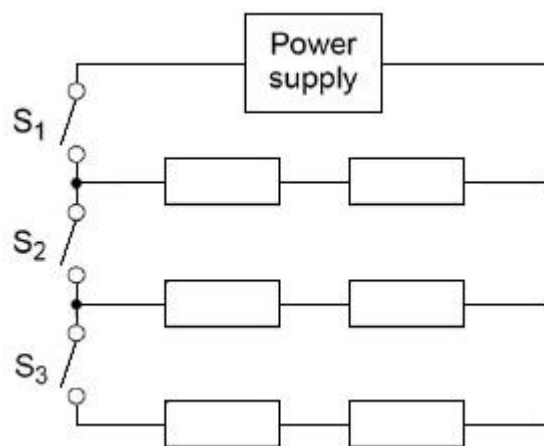


**Questions are for both separate science and combined science students****Q1.****Figure 2** shows the circuit diagram for the hair straighteners.

Each resistor represents a heating element.

The power output of the hair straighteners can be changed by closing different switches.

**Figure 2**


- (a) Why do the hair straighteners **not** turn on when only switch  $S_2$  is closed?

---

---

**(1)**

- (b) **Figure 3** shows the hair straighteners circuit with switch  $S_1$  closed.

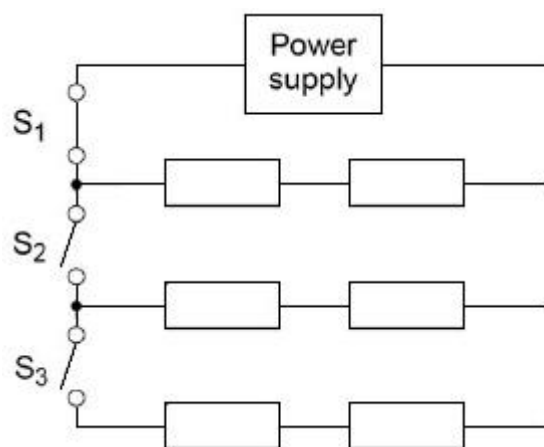**Figure 3**Switch  $S_2$  and switch  $S_3$  are then closed at the same time.

Explain what happens to the power output of the power supply.

---

---

---

---

---

---

---

---

**(3)**

**(Total 4 marks)**