

- 1 (a) (i)  $(I =) V/R$  OR  $6/(12 + 4)$  OR  $6/16$   
0.38 A/0.37 A A1
- (ii)  $1/R = 1/R_1 + 1/R_2$   
OR  $(R =) R_1 R_2 / (R_1 + R_2)$   
OR above with numbers substituted C1
- $R = 3 (\Omega)$  C1
- $(I = 6/3 =) 2(.0) A$  A1
- OR ALTERNATIVE METHOD:  
 $6/12$  (C1)
- $+ 6/4$  (C1)
- $2(.0) A$  (A1)
- (b) (i)  $R \propto l$  (in words or symbols)  
OR directly proportional OR e.g.  $R$  doubles when  $l$  doubles B1
- (ii)  $R \propto 1/A$  (or with words)  
OR inversely proportional OR e.g.  $R$  doubles when  $A$  halves B1
- (c)  $4/12$  OR  $4:12$  OR  $1/3$  OR  $1:3$  OR  $0.33$  B1

**[Total: 8]**

- 2 (a) 4.5V ignore sign B1
- (b)  $1/R_p = 1/R_1 + 1/R_2$   
 OR  $(R_p =) R_1 R_2 / (R_1 + R_2)$  words, symbols or numbers C1
- $R = (1/(1/1 + 1/5)) = 0.83\Omega$  A1
- (c)  $V = IR$  in any form OR  $V/R$  words, symbols or numbers C1
- use of total e.m.f. as  $V$  AND series resistance as  $R$   
 OR 4/5 of total emf seen OR 1/6 of total current seen C1
- $(I = 4.5/5 =) 0.90\text{ A}$  accept 0.9 e.c.f. from (a) A1
- (d) 1.5V ignore sign B1
- [Total: 7]**

- 3 (a)  $(P =) VI$  OR  $230 \times 3.5$  C1
- 805/810 W A1
- (b)  $(I_Y =) 7.0\text{ (A)}$   
 alternative method:  $(R_X =) V/I$  OR  $230/3.5$  OR  $66/65.7(1429)$  C1
- $(I_{\text{Tot}} =) 10.5\text{ (A)}$   
 alternative method:  $((R_Y =) 230/7.0$  OR  $66/2$  OR  $65.7(1429)/2$  OR  $33/32.9/32.85714)$  C1
- $(R =) V/I$  OR  $230/10.5$   
 alternative method:  $(R =) R_1 R_2 / (R_1 + R_2)$  OR  $2159/98.57$   
 OR  $1/R = 1/R_1 + 1/R_2$  OR  $1/R = 1/65.7 + 1/32.9$  C1
- 22/21.9(0476)  $\Omega$  A1
- [Total: 6]**

- 4 (a) (lamps) stay on/have same brightness as before/nothing happens B1  
 (lamps) still connected to supply/have same voltage as before/are connected in parallel B1
- (b) line 1: on line 2: off I B2  
 deduct one mark for e.e.o.e.
- (ii) when either switch is operated, the state of the lamp changes. B1

[Total: 5]

- 5 (a) one mark for each correct entry in table: B3

resistor	res	current	potential difference	power
			$IR$	
		$I$		$2I^2R$

- (b) (i) ( $P = IV = 750 \times 11000 =$ )  $8.3 \times 10^6 \text{ W}$  (8300 kW) B1
- (ii) ( $V = IR = 750 \times 1.5 =$ ) 1100 V B1
- (iii) (voltage to factory = 11 000 – 1125 =) 9875 V C1  
 (power supplied to factory =)  $9875 \times 750$  A1  
 $7.4 \times 10^6 \text{ W}$  OR 7400 kW A1  
**OR**  
power loss in cables =  $I^2R$  OR  $750^2 \times 1.5$  (C1)  
 (=)  $8.44 \times 10^5 \text{ (W)}$  (A1)  
 (power to factory =  $8.25 \times 10^6 - 8.44 \times 10^5 =$ )  $7.4 \times 10^6 \text{ W}$  OR 7400 kW (A1)

[Total: 8]

- 6 (a) 6.0 V B1
- (b) (i) coulomb (IGNORE C) B1
- (ii)  $(Q =) It$   
**OR**  $0.25 \times 12 \times 60$  **OR**  $0.25 \times 720$  **OR**  $0.25 \times 12$  **OR** 3.0 **OR**  $0.25 \times 60$  **OR** 15  
 180(C) C1  
 A1
- (iii)  $(R =) V/I$  or  $6.0/0.25$  or 24.0 e.c.f. from (a)  
**OR**  
 $(V =) IR$  **OR**  $0.25 \times 16$  **OR** 4.0 e.c.f. from (a) C1
- 8.0  $\Omega$  A1
- (c)  $R \propto l$  **OR** 8.0 **OR** 16/2 C  
 $R_1 R_2 / (R_1 + R_2)$  **OR**  $1/R = 1/R_1 + 1/R_2$  **OR** 64/16 **OR**  $1/R = 1/8 + 1/8$  C  
 4.0  $\Omega$  A1

[Total: 9]

- 7 (a) (i) all lamps off
- (ii) 12  $\Omega$  lamps (only) on B1
- (iii) 4  $\Omega$  lamps (only) on
- (b) 12 V B1
- (ii)  $I = V/R$  in any form **OR**  $V/R$  **OR** 12/12 C1  
 1.0 A **OR** 1 A A1  
 e.c.f. from (b)(i)
- (c) current in 4  $\Omega$  lamp = 3 (A) (current in 12  $\Omega$  lamp is in (b)(ii)) C  
 $(P =) IV$  **OR**  $I^2 R$  C1  
 $(P =) 36$  W for 4  $\Omega$  lamp;  $P = 12$  W for 12  $\Omega$  lamp A1  
 e.c.f. from (b)(ii)  
**OR**  
 $(P =) V^2/R$  (C1)  
 $(P =) 12^2/4 = 36$  W for 4  $\Omega$  lamp **OR**  $12^2/12 = 12$  W for 12  $\Omega$  lamp (C1)  
 $(P =) 12^2/4 = 36$  W for 4  $\Omega$  lamp **AND**  $12^2/12 = 12$  W for 12  $\Omega$  lamp (A1)  
**OR**  
 $(P =) V^2/R$  (B1)  
 Same V for all lamps (M1)  
 4  $\Omega$  lamp has higher power / 12  $\Omega$  has lower power (A1)

[Total 7]