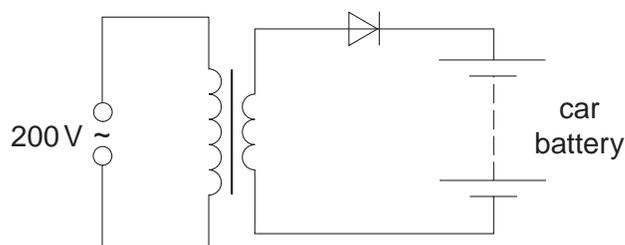


1 Fig. 8.1 shows a car battery being charged from a 200V a.c. mains supply.



**Fig. 8.1**

(a) State the function of the diode.

.....  
 ..... [1]

(b) The average charging current is 2.0A and the battery takes 12 hours to charge fully.

Calculate the charge that the battery stores when fully charged.

charge stored ..... [2]

(c) The battery has an electromotive force (e.m.f.) of 12V and, when connected to a circuit, supplies energy to the circuit components.

State what is meant by an *electromotive force of 12 V*.

.....  
 .....  
 ..... [2]

**(d) (i)** In the space below, draw a circuit diagram to show how two 6.0V lamps should be connected to a 12V battery so that both lamps glow with normal brightness. [1]

**(ii)** The power of each lamp is 8.0W. Calculate the current in the circuit.


current = ..... [2]

**(iii)** Calculate the energy used by the two lamps when both are lit for one hour.

energy = ..... [2]

[Total: 10]

2 Fig. 8.1 shows part of a low-voltage lighting circuit containing five identical lamps.

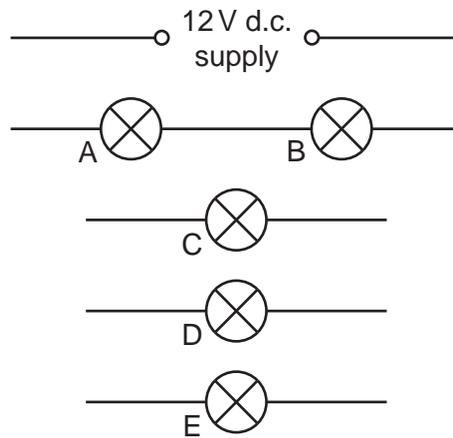

**Fig. 8.1**

- (a) Complete the circuit, by the addition of components as necessary, so that
- (i) the total current from the supply can be measured,
  - (ii) the brightness of lamp E only can be varied,
  - (iii) lamps C and D may be switched on and off together whilst lamps A, B and E remain on. [4]
- (b) All five lamps are marked 12V, 36W. Assume that the resistance of each lamp is the same fixed value regardless of how it is connected in the circuit.

Calculate

- (i) the current in one lamp when operating at normal brightness,

current = ..... [1]

(ii) the resistance of one lamp when operating at normal brightness,

resistance = ..... [1]

(iii) the combined resistance of two lamps connected in parallel with the 12V supply,

resistance = ..... [1]

(iv) the energy used by one lamp in 30s when operating at normal brightness.

energy = ..... [1]

(c) The whole circuit is switched on. Explain why the brightness of lamps A and B is much less than that of one lamp operating at normal brightness.


.....

.....

..... [2]

[Total: 10]

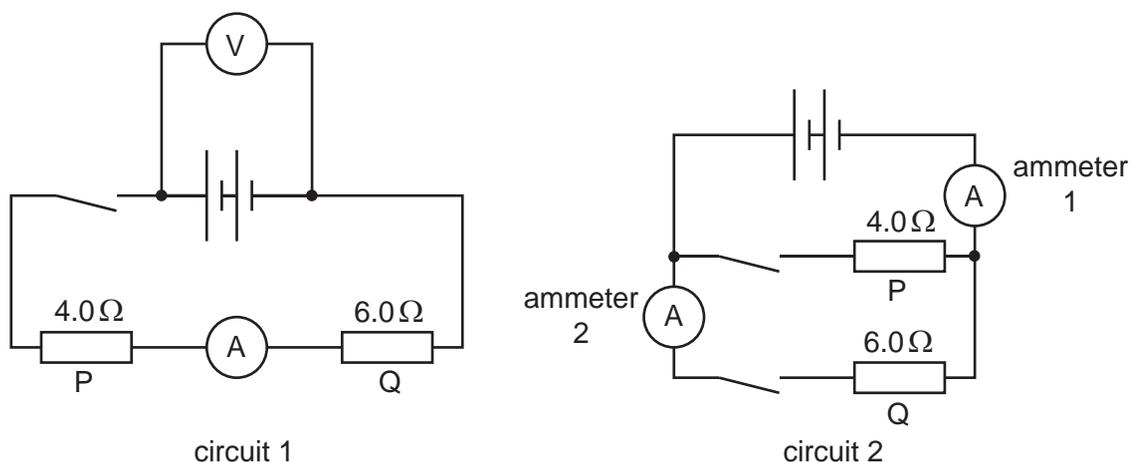3 Fig. 8.1 shows two electrical circuits.



The batteries in circuit 1 and circuit 2 are identical.

**Fig. 8.1**

(a) Put ticks in the table below to describe the connections of the two resistors P and Q.

	series	parallel
circuit 1		
circuit 2		

[1]

(b) The resistors P and Q are used as small electrical heaters.

State two advantages of connecting them as shown in circuit 2.

advantage 1 .....

advantage 2 ..... [2]

(c) In circuit 1, the ammeter reads 1.2A when the switch is closed.

Calculate the reading of the voltmeter in this circuit.

voltmeter reading = ..... [2]

(d) The two switches in circuit 2 are closed. Calculate the combined resistance of the two resistors in this circuit.

combined resistance = ..... [2]

(e) When the switches are closed in circuit 2, ammeter 1 reads 5A and ammeter 2 reads 2A.

Calculate

(i) the current in resistor P,

current = ..... [1]

(ii) the power supplied to resistor Q,


power = ..... [1]

(iii) the energy transformed in resistor Q in 300s.

energy = ..... [1]

[Total: 10]

4 Fig. 8.1 shows an electrical circuit.

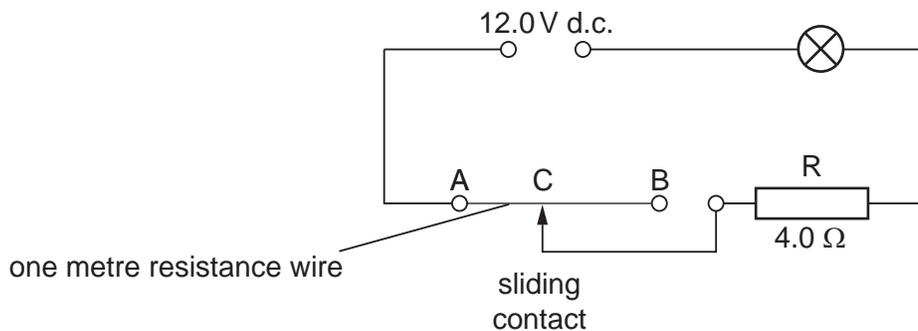

**Fig. 8.1**

The resistance of the lamp is  $4.0\Omega$  when it is at its normal brightness.

- (a) The lamp is rated at 6.0V, 9.0W.  
Calculate the current in the lamp when it is at its normal brightness.

current = .....[2]

- (b) The sliding contact C is moved to A. The lamp lights at its normal brightness.  
Calculate

- (i) the total circuit resistance,

resistance = .....[1]

- (ii) the potential difference across the  $4.0\Omega$  resistor R.

potential difference = .....[1]

- (c) The sliding contact C is moved from A to B.

- (i) Describe any change that occurs in the brightness of the lamp.

.....[1]

- (ii) Explain your answer to (i).

.....

.....[2]

**(d)** The 1 m wire between A and B, as shown in Fig. 8.1, has a resistance of  $2.0\ \Omega$ . Calculate the resistance between A and B when

**(i)** the 1 m length is replaced by a 2 m length of the same wire,

resistance = .....[1]

**(ii)** the 1 m length is replaced by a 1 m length of a wire of the same material but of only half the cross-sectional area.

resistance = .....[1]

[Total : 9 ]