

- 1 (a) Example: e.g. battery: (chemical to) electrical
 engine: (chemical to) kinetic / mechanical
 fire: (chemical to) thermal / heat
 (human) body: (chemical to) heat / kinetic B1
- (b) (i) ($P = IV$) OR in words OR 0.27×17
 $= 4.59 \text{ W}$ at least 2 s.f. C1
 A1
- (ii) (K.E. =) efficiency \times input OR 0.35×4.59 C1
 $= 1.61 \text{ J}$ or Nm at least 2 s.f. A1
- (iii) 1. $d = m/V$ OR ($m = V \times d$) OR in words OR 0.00014×1000
 $= 0.14 \text{ kg}$ C1
2. P.E. gained = K.E. lost OR $mgh = \frac{1}{2} mv^2$
 OR $0.14 \times 10 \times h = 1.61$ OR 1.6 C1
 $h = 1.15 \text{ m}$ OR 1.14 m at least 2 s.f. A1
- OR
 $\frac{1}{2} mv^2 = 1.61$ OR
 $v^2 = 2 \times 1.61 / 0.14 = 23$ OR $v^2 = 2 \times 1.6 / 0.14 = 22.86$ (C1)
 $(h =) v^2/2g = 23/20 = 1.15 \text{ m}$ OR $(h =) 22.86/20 = 1.14 \text{ m}$ (A1)

[Total: 9]

- 2 (a) (i) total $R = 320 (\Omega)$ or V per lamp = $6 (\text{V})$
 $I = (240/320 \text{ or } 6/8 =) 0.75 \text{ A}$ ecf from previous line A1 [2]
- (ii) use of $P = VI$ OR I^2R OR V^2/R C1
 4.5 W ecf from (a)(i) A1 [2]
- (b) resistance of each lamp = $8 \times 1.05 = 8.4 (\Omega)$
 total $R = 240/0.9 = 266.7 (\Omega)$ OR V per lamp = $8.4 \times 0.9 = 7.56 (\text{V})$ B1
 no. of lamps (= $266.7/8.4$) = 31.7 OR (= $240/7.56$) = 31.7 B1
 max. no. of failed lamps = 8 B1
 accept reverse logic [4]

[Total: 8]

- 3 (a) any three from:
 use a strong(er) magnet
 increase the number of coils in the solenoid / turns of solenoid closer together
 move the magnet fast(er).
 place iron core in the solenoid
 use thick(er) wire / low(er) resistance wire for solenoid max B3
- (b) (i) $N_P/N_S = V_P/V_S$ OR $200/800 = V_P/24$ OR $V_P = N_P V_S / N_S$ C1
 OR $V_P = 200 \times 24 / 800$ A1
 6.0V
- (ii) $I_P V_P = I_S V_S$ OR $I_P N_P = I_S N_S$ OR $I_P = I_S V_S / V_P$ OR $I_P = I_S N_S / N_P$ C1
 OR $I_P = (0.5 \times 24) / 6$ OR $I_P = (0.5 \times 800) / 200$ C1
 2(.0)A
 allow ecf from (b)(i) A1 [7]
- 4 (a) (i) 0(A) / zero Unit penalty if wrong unit B1
- (ii) 12V B1
- (b) (i) V / R OR $V = IR$ in any form, letters, words or numbers C1
 0.5A A1
- (ii) $8 \times$ candidate's (i) OR $8/24 \times 12$ C1
 4V OR 4.0V e.c.f. A1
- (c) $1/R_1 + 1/R_2 = 1/R$ OR $R = R_1 R_2 / (R_1 + R_2)$ in any form B1
 5.3(Ω) OR $5\frac{1}{3}$ (Ω) OR $16/3$ (Ω) C
 12 / candidate's R C1
 2.25A c.a.o. A1
- Alternatively: $12/16 (= 0.75)$ OR $12/8 (= 1.5)$ C1
 $12/16 (= 0.75)$ AND $12/8 (= 1.5)$ C1
 Currents added C1
 2.25A c.a.o. A1 [10]

- 5 (a) all 4 lights in parallel with supply and none in series B1
 master switch in a place where it will work (cannot score if no supply or if short circuit) B1
 one switch for 2 lights in living room AND one for bathroom B1
 AND one for bedroom
- (b) (i) $W = V \times I$ or $100 = 200 \times I$ in any form C1
 0.5 A or 0.5 a A1
- (ii) $I \times t$ or 0.5×60 e.c.f. C1
 30 C or 30 c e.c.f. A1
- (c) (i) 135 W B1
- (ii) any power \times any time (words or symbols or numbers) C1
 NOTE: 280 (W) is the total power of lamps in house, so counts as "power"
- 486 000 J or 486 kJ or 0.135 kWh accept lower case units A1
 NOTE: $45 \times 3600 = 162000$ J gets e.c.f. from (i)

[10]

- 6 (a) changes a.c. to d.c. OR rectifies a/c OR allows current to flow one way only B1
 OR prevents current flowing backward
- (b) $I \times t$ or 2×12 or $2 \times 12 \times 60 \times 60$ or amps \times seconds C1
 24 Ah or 86 400 C or 86 000 C A
- (c) emf = J/C OR energy converted/work done per unit charge/coulomb C1
 OR W/A OR volts/p.d. when no current in circuit
 12 J of energy are delivered/needed for every coulomb of charge
 OR 12 W is the power to drive a current of 1 A A
- (d) (i) series connection shown, any recognisable symbols B1
- (ii) total power = 16 W OR 8/6 C1
 1.33 A accept fraction c.a.o. A1
- (iii) any power \times any time or $16 \times 60 \times 60$ or IVt or $8 \times 60 \times 60$ C1
 57 600 J or 0.016 kWh or 28 800 J or 0.008 kWh

[10]

7	(a)	switch in correct position	B1	[1]
	(b)	(i) rheostat/variable resistance symbol drawn	B1	
		(ii) dot and R in line to 12 W lamp	B1	[2]
	(c)	Question deleted		
	(d)	R = V/I or $12/.3$ = 4Ω	C1 A1	[2]
	(e)	(i) parallel circuit/all lamps connected separately across the 12V	B1	
		(ii) 4 A	A1	[2]
				[Total: 7]