

Question	Answer	Marks	Guidance
1 a i	0.72 (volts) (2) but if answer incorrect 0.7185 or 0.718 or 0.719 or 0.7 (volts) (1)	2	Allow 0.15 x 4.79 (1)
ii	D (1)	1	if answer line blank allow correct answer circled or underlined more than one answer = 0 marks
b	Any two from: increase the current by one from <ul style="list-style-type: none"> - moving the slider clockwise or upwards or to the left - having less wire / fewer coils in circuit [1] decrease the current by one from <ul style="list-style-type: none"> - moving the slider anticlockwise or downwards or to the right - having more wire / coils in circuit [1] increasing length increases resistance / increasing resistance decreases current / ORA [1]	2	allow labelled arrows or indications on diagram to indicate correct directions for upwards allow towards the power supply for downwards allow away from the power supply Allow changing length changes resistance [1] But increasing length decreases resistance / ORA [0] Allow changing resistance changes current [1] But increasing resistance increases current / ORA [0]
	Total	5	

Question	Answer	Marks	Guidance			
2 a C O M M O N	<table border="1" style="margin-left: 20px;"> <tr><td style="text-align: center;">82</td></tr> <tr><td style="text-align: center;">104</td></tr> <tr><td style="text-align: center;">128</td></tr> </table> <p style="text-align: right;">(1)</p>	82	104	128	1	all correct for 1 mark
82						
104						
128						
C O M M O N	b i I_b is (always much) smaller than I_c / ORA [1]	1				
C O M M O N	ii (idea that) a small base current is needed to switch on the transistor (1) (this allows) a large current through the transistor (1)	2	allow higher level answers e.g. transistors have a high gain (1)			

Question	Answer	Marks	Guidance
c	<p>max two from any of these advantages:</p> <p>robot can do jobs that are more: boring / dangerous / unpleasant / intricate / labour intensive / hygienic / take longer</p> <p>Other advantages are that robots are safer / stronger / more efficient / faster</p> <p>Other advantages that robots don't get sick / don't take holidays / don't get paid / don't make human errors / don't take breaks / don't need feeding / don't get tired</p> <p>max two from any of these disadvantages:</p> <p>robots may be limited in decision making / need reprogramming / expensive to buy or maintain / robots take peoples jobs / may take over (the world) / dangerous to humans if a fault develops (1)</p>	3	<p>Ignore can do repetitive work</p> <p>Ignore robots do jobs that humans don't want to do</p>
Total		7	

Question	Answer	Marks	Guidance
3 a	<p>LDR resistance decreases as light (level) increases / AW [1]</p> <p>Thermistor (NTC) resistance decreases as temperature increases / AW [1]</p>	2	<p>allow ORA [1]</p> <p>allow ORA [1]</p> <p>allow heat for temperature</p> <p>allow Thermistor PTC resistance increases as temperature increases [1]</p>
b	<p>Any two from current passes:</p> <p>Idea of threshold voltage reached / AW [1]</p> <p>in one direction / AW [1]</p> <p>when the voltage is positive / resistance is low/AW [1]</p>	2	<p>e.g. if voltage is high enough/ 0.6V</p> <p>Allow (the idea that) current is correct direction for the diode [1]</p> <p>allow no current when voltage is negative [1]</p> <p>allow (idea that) circuit diagram shows diode in forward bias / current direction is L to R / anticlockwise for this diode [1]</p>
Total		4	

Question	Answer	Marks	Guidance
4 a	7.5 (ohms) [2] but if answer incorrect correct values of voltage and current from graph [1]	2	correct values e.g. 3 and 0.4 or 6 and 0.8
b	E (no marks) Idea that longer conductors have a greater resistance [1] (idea that) the line with the shallowest / least gradient has the greatest resistance [1]	2	If E NOT chosen [0] Longer length has lower current [1] allow credit for candidates who calculate the resistance of E as 200 (Ω) [1]
c	mistakes are: electrons not protons are the charge carriers atoms vibrate more not less increases the resistance of the conductor not decreases it	2	allow mistakes indicated on the text three mistakes corrected [2] one or two mistakes corrected [1]
Total		6	

Question			Answer	Marks	Guidance
5	(a)	(i)	0.15 (amps) (3) but if answer incorrect (I =) $0.75 / 5$ (2) or 5 or 4.8 to 5.2 (ohms stated as the resistance) (1)	3	allow answer in the range of 0.144 – 0.156 (amps) (3) allow 5 in range of 4.8 – 5.2 allow 5 (ohms) seen (even in an incorrect calculation) (1) eg. $5 / 0.75$ (1) eg. 5 (taken from graph / slope of graph) (1)
		(ii)	as length increases current reduces / AW / ora (1)	1	allow inversely proportional ignore resistance / faster or stronger current
	(b)		straight line (by eye) on graph starting at / pointing towards (0,0) with a steeper gradient than original line (1)	1	curved line (by eye) scores (0)
Total				5	

Question		Answer	Marks	Guidance
6	(a)	resistance decreases (1) brightness of lamp / current increases (1)	2	ignore weaker resistance ignore faster / stronger current But resistance increases (0) so brightness of lamp / current decreases (1)
	(b) (i)	0.92 (Ω) (2) but if answer is incorrect $\frac{1}{R_T} = \frac{1}{2} + \frac{1}{3}$ (1) or $\frac{1}{R_T} = 0.5 + 0.33 + 0.25$ (1)	2	allow 0.92(307692) (2) allow 0.9 (2) allow $\frac{12}{13}$ (Ω) (2)
	(ii)	4.3 (amps) (2) but $\frac{4}{0.92}$ (1)	2	allow 4.30 to 4.45 (2) allow ecf from bi (2) eg for ecf of 1.08 - allow 3.7 (2) eg for ecf of 9 - allow 0.44 or 0.4 (2) allow 4 / answer to bi (1) eg 4/1.08 (1) allow 4.30 to 4.45 (2) allow $\frac{4}{\text{answer to b(i)}}$ (1)
	(c)	$I_e = 0.60 \text{ mA}$ (1)	1	Allow 0.6 (1)
Total			7	