

Simple Circuits (F)

1. Which voltage is the maximum voltage made when **four** 1.5 V cells are connected in **series**?


- A 0 V
- B 1.5 V
- C 3.0 V
- D 6.0 V

Your answer

[1]

2. A student has 3 identical resistors. She arranges them in four different ways.


A

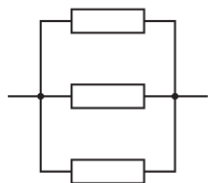


B



C

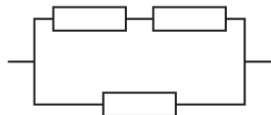

D

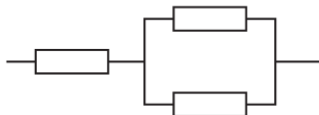





Which arrangement has the **most** resistance?

Your answer

[1]

3. A student investigates how current and potential difference vary in different components.

Look at the graphs of her results.

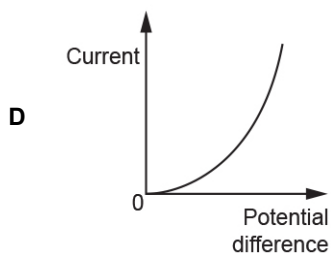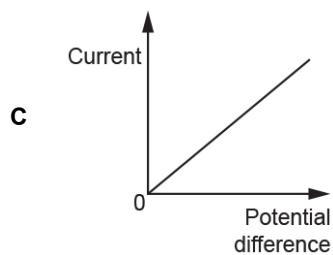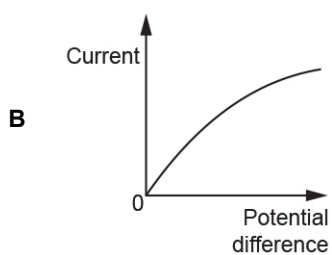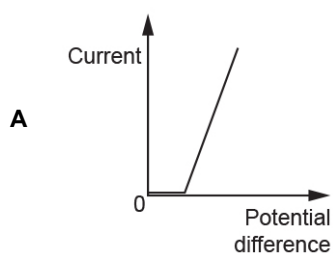





Which graph shows a filament lamp?

Your answer

[1]

4. A student sets up four different circuits. He uses identical lamps and the same cell.

Look at the diagrams of his circuits.

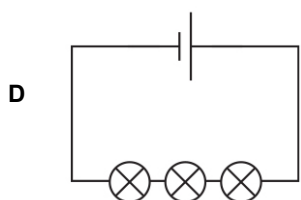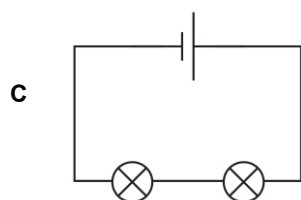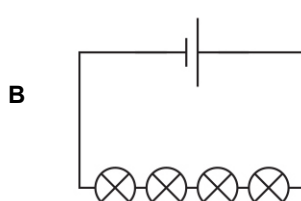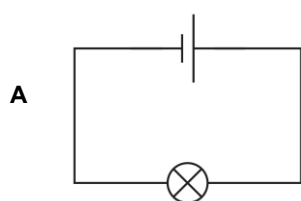

Which circuit has the brightest lamp(s)?

Your answer

[1]

5. The table shows the current and potential difference for four different lamps.

Which lamp has the highest **power**?





Use the equation: power = potential difference \times current

	Current (A)	Potential difference (V)
A	2	5
B	3	4
C	4	2
D	5	1

Your answer

[1]

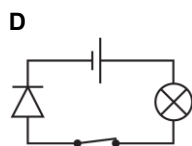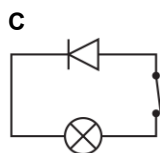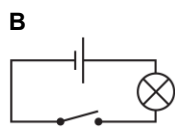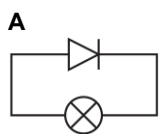6. A student sets up four electrical circuits.




Identify in which circuit the lamp will light up.

Your answer

[1]

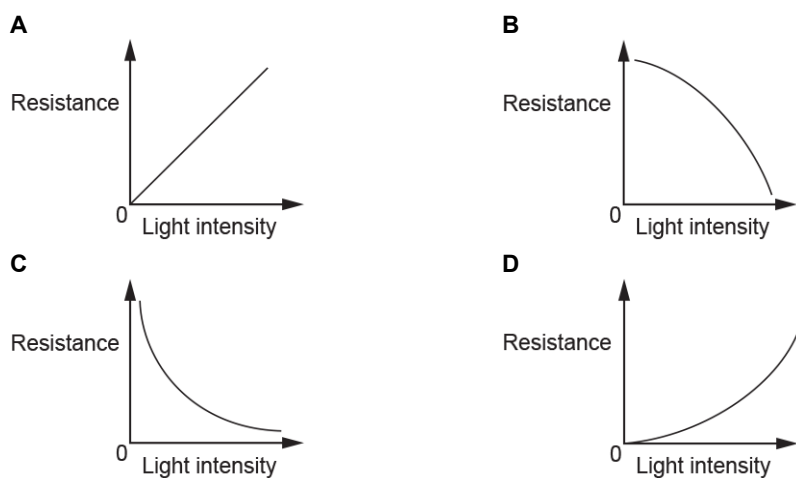7. A student investigates how the resistance of a light dependent resistor (LDR) changes with light intensity.



Which graph shows the correct relationship between the resistance of an LDR and light intensity?

Your answer

[1]

8. Which item uses the most power?

Use the equation: power = potential difference \times current

	Item	Current (A)	Potential difference (V)
A	Calculator	0.1	3
B	Mobile Phone	1.0	5
C	Radio	0.5	12
D	Torch	1.2	6

Your answer

[1]

9 (a). A student uses four electrical appliances for different lengths of time.

Look at the table.

Appliance	Power (W)	Time used (hours)
Hair dryer	1500	0.3
TV	100	5
Toaster	2000	0.2
Light bulb	10	12

i. Which appliance uses the **most** energy?

..... [1]


ii. Which appliance uses the **least** energy?

..... [1]

(b). Here are three different components and their use in the home.

Match the component to its correct use.

One has been done for you.

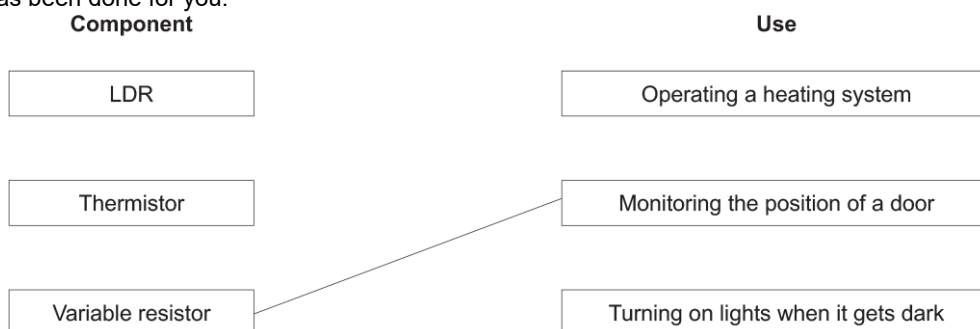

[2]

(c). A charge of 44 000 C flows through a light bulb. The potential difference is 230 V.


Calculate the energy transferred.


Use the equation: Charge = Energy ÷ Potential difference

Record your answer to **2** significant figures.

Answer = J [4]

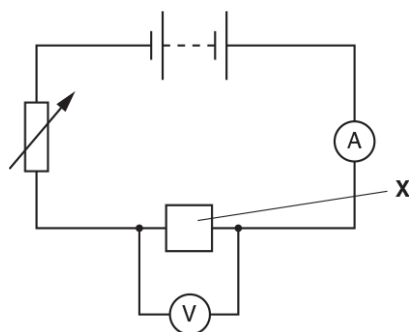10 (a). A student builds a circuit to investigate the resistance of component X.



- i. What is the name of this component? 


----- [1]

- ii. Why is this component needed in this circuit?

----- [1]

(b). The student uses the circuit to take current and potential difference readings.

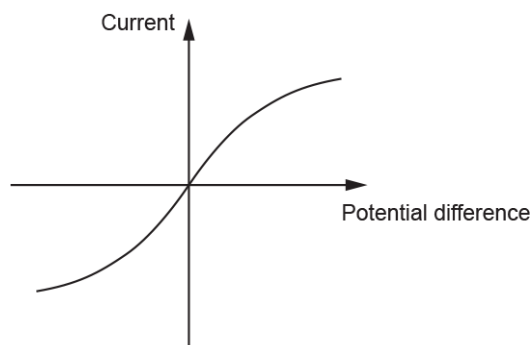The student plots a graph of her results.



- i. Look at the graph.
What is component X in the circuit?

----- [1]

- ii. The resistance of component X varies as the potential difference changes.
Describe **how** the graph shows this and explain **why** this happens.

----- [3]

(c). Component **X** has a resistance of $16\ \Omega$ when a current of $0.25\ \text{A}$ flows.

- i. Calculate the potential difference across component **X**.

Use the equation: Potential difference = Current \times Resistance

Answer = V [2]

- ii. Calculate the power of component **X** when a current of $0.25\ \text{A}$ flows.

Answer = W [3]

11. A domestic wind turbine has a power rating which varies from $1.0\ \text{kW}$ to $3.0\ \text{kW}$.

- i. The domestic wind turbine has an electrical resistance of $23\ \Omega$.

It generates a current of $11\ \text{A}$ on a windy day.

Calculate the **power** output in kW of the turbine on this day.

Answer = _____ kW [4]

- ii. Suggest why the manufacturer gives a range for the power rating of the wind turbine.

----- [1]


- iii. Using just **one** domestic wind turbine may be an unreliable source of power for a house.

State a reason why.

----- [1]

12 (a). A student sets up a circuit to find out the resistance of an unknown resistor. The student makes **three** mistakes in their circuit.

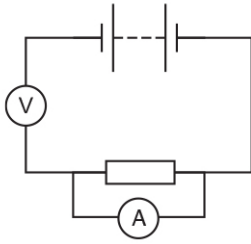Look at the circuit diagram of their experiment.



i. Write down the **three** mistakes the student makes.

1

2

3

[3]

i. For **one** of the mistakes identified in (i) describe how the student can fix the error.

[1]

(b). The student finds that the current is 20 mA when the potential difference is 4.0 V.

Calculate the **resistance** of the unknown resistor.

Include the **unit** for resistance in your answer.

Use the equation: resistance = potential difference ÷ current.

Resistance = Unit = [4]

13 (a). A TV has the label below on it.

OCR TV Voltage: 230 V Power: 65 W Frequency: 50 Hz
--

Calculate the **current** in the TV when it is turned on.

Use the equation: power = potential difference \times current

Give your answer to **2** significant figures.


Current = A [4]

(b). The TV is turned on for 30 minutes.

Calculate the energy transferred by the TV.

Energy used = J [4]

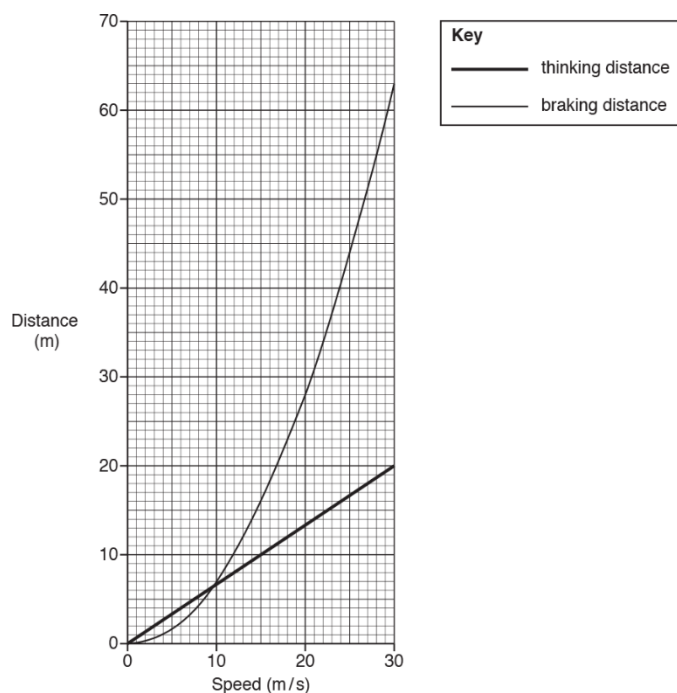14. The graph shows thinking and braking distances for a car at different speeds.



Describe how **thinking distance** varies with increasing speed.

Use data from the graph in your answer.

[2]

15(a). A student sets up the circuit in **Fig. 17.1** to investigate the resistance of a lamp.

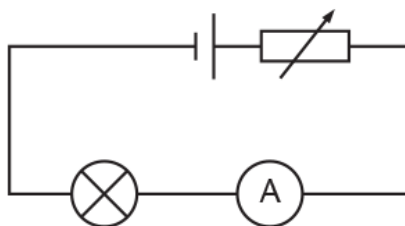


Fig. 17.1

- i. The student also needs to add a voltmeter to the circuit.

On **Fig. 17.1** draw where the voltmeter should be connected.

[2]

- ii. The student takes readings of potential difference and current and records them in **Table 17.1**.

Potential difference (V)	Current
1.0	1.000
2.0	1.9
3.0	2.7
4.0	3.2
5.0	3.5

Table 17.1

There are **two** mistakes in the results table.

Write down the **two** mistakes and suggest how they could be corrected.

Mistake 1:

Correction 1:

Mistake 2:

Correction 2:

[4]

- iii. Calculate the resistance of the lamp when the potential difference is 4.0 V in **Table 17.1**.

Use the equation: potential difference = current \times resistance

Resistance = Ω **[3]**

(b). The student plots the results from **Table 17.1** on the graph in **Fig. 17.2**.

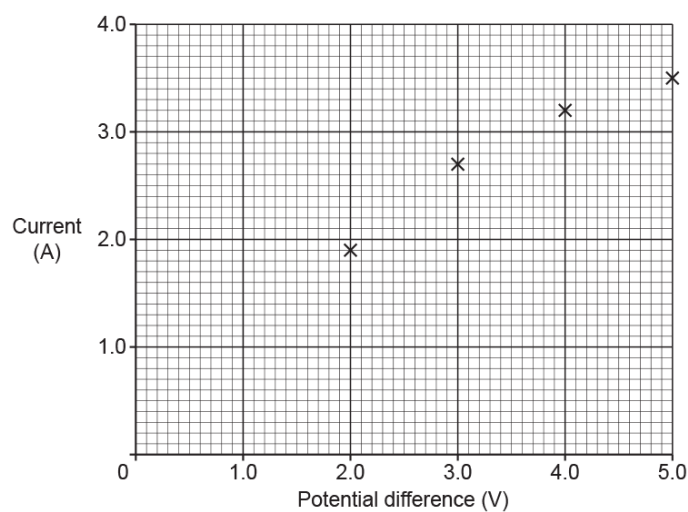


Fig. 17.2

- i. Plot the missing point at 1.0 V on the graph **and** draw a line of best fit.

[2]

- ii. Describe the relationship between potential difference and current.

Use data from the graph to support your answer.

[2]


- iii. Explain how you could use the circuit in **Fig. 17.1** to investigate the resistance of a fixed resistor instead of a lamp.

[2]

- iv. Explain how and why the graph in **Fig. 17.2** would look different for a fixed resistor at a constant temperature.

[2]

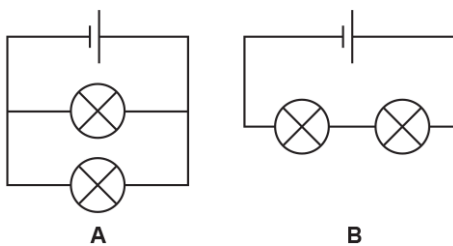16. A student investigates if lamps are brighter in a series circuit or a parallel circuit. He sets up two different circuits, **A** and **B**.



State which circuit will have the brightest lamps and explain why.

In your answer, include the variables that the student will need to control in this experiment.

[6]

17. Calculate the charge when 200 J of energy is transferred with a potential difference of 40 V.

Use the equation: energy transferred = charge \times potential difference

Charge = C **[3]**

END OF QUESTION PAPER