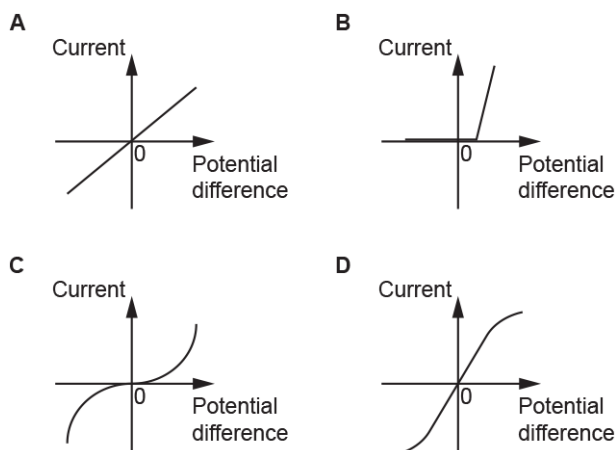


## Simple Circuits (H)

1. A student investigates four different electrical components.

She plots current-potential difference graphs for the components.



Which of the above shows the characteristic graph for a diode?

Your answer

[1]

2. Voltage is increased before transmission through the National Grid.

It is increased from 25 000 V up to 400 000 V. This increases the voltage 16 times.

i. How much would this increase in voltage affect the current?

-----

----- [2]

ii. Use the formula: **power = current<sup>2</sup> × resistance**


to explain why this voltage increase is important to power loss in transmission cables.

-----


-----

----- [2]

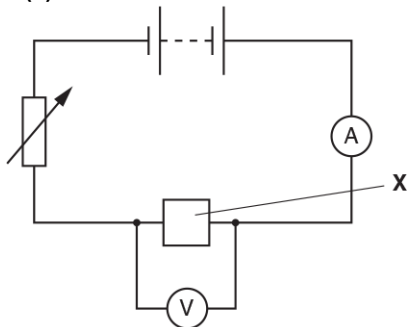**3 (a).** A student builds a circuit to investigate the resistance of component **X**.



i. What is the name of this component?

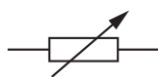


----- [1]

ii. Why is this component needed in this circuit?

----- [1]

**(b).** The student uses the circuit to take current and potential difference readings.

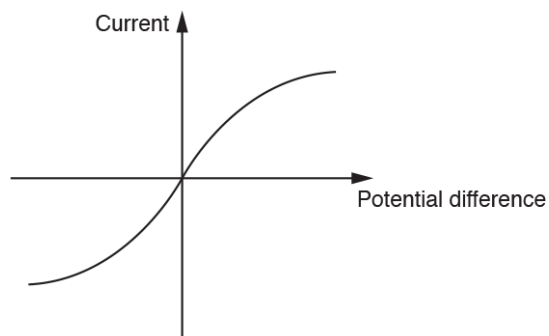The student plots a graph of her results.



i. Look at the graph. What is component **X** in the circuit?

----- [1]

ii. The resistance of component **X** varies as the potential difference changes.

Describe how the graph shows this and explain why this happens.

----- [3]

(c). Component **X** has a resistance of  $16\ \Omega$  when a current of  $0.25\ \text{A}$  flows.

i. Calculate the potential difference across component **X**.

Use the equation: Potential difference = Current  $\times$  Resistance


Answer = ..... V [2]

ii. Calculate the power of component **X** when a current of  $0.25\ \text{A}$  flows.

Answer = ..... W [3]

4 (a). Two students investigate the resistance of a wire.

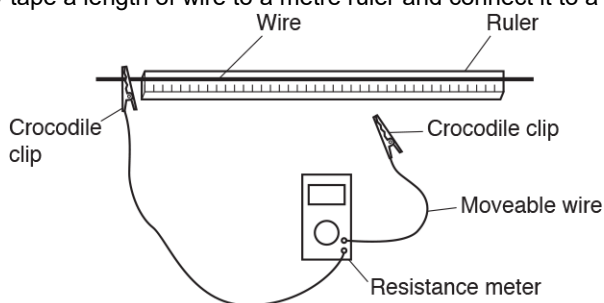They tape a length of wire to a metre ruler and connect it to a resistance meter using crocodile clips.



Look at their results.

Length of wire (cm)	Resistance ( $\Omega$ )			Mean
	Attempt 1	Attempt 2	Attempt 3	
25	8.8	8.3	8.5	8.533
50	16.2	16.1	16.4	16.4
75	23.5	23.8	18.7	23.7
100	30.8	31.1	31.0	31.0

i. Describe the pattern shown by these results.

Use data in your answer.

-----

-----

-----

[2]

- ii. The students made **two** mistakes when they recorded their results and completed the table.

Identify the mistakes **and** explain what they should have done.

-----  
-----  
----- [2]

- iii. The students have correctly handled an anomaly in their results.

Identify the anomaly and explain how it was correctly handled.

-----  
-----  
----- [2]

- iv. The students plan to plot a graph of mean resistance against length.

What would you expect a graph of these results to look like?

-----  
-----  
----- [2]

(b).

- i. The actual mean resistance values are more than expected.

Suggest **two** possible errors with the experiment.

-----  
-----  
----- [2]

- ii. For **one** of the errors, suggest how the experimental procedure could be improved.

-----  
----- [1]

5. A domestic wind turbine has a power rating which varies from 1.0 kW to 3.0 kW.

- i. The domestic wind turbine has an electrical resistance of  $23 \Omega$ .

It generates a current of 11 A on a windy day.

Calculate the power output in kW of the turbine on this day.

Answer = ..... kW [4]

- ii. Suggest why the manufacturer gives a range for the power rating of the wind turbine.

.....  
..... [1]

- iii. Using just **one** domestic wind turbine may be an unreliable source of power for a house.

State a reason why.

.....  
..... [1]

6. A TV works with a 12.0 V battery. It has a current of 3.19 A.

Calculate the power rating of the TV.

Power = ..... W [3]

7 (a). Energy is transferred at high voltages in the national grid.

This house is near to a transmission line.



Explain why radio waves may be produced by the transmission line.

-----

-----

----- [2]

(b). Explain why it is more efficient to transfer energy at high voltages.

-----

-----

----- [2]

(c). The transmission line has a power loss of 6.156 kW.

Its resistance is 15.39  $\Omega$ .

Calculate the current in the transmission line.

Current = ..... A [5]

8 (a). A TV has the label below on it.

**OCR TV**

Voltage: 230 V

Power: 65 W

Frequency: 50 Hz

Calculate the **current** in the TV when it is turned on.

Use the equation: power = potential difference  $\times$  current

Give your answer to **2** significant figures.

Current = ..... A [4]

**(b).** The TV is turned on for 30 minutes.


Calculate the energy transferred by the TV.

Energy used = ..... J [4]

**9 (a).** A student investigates the electrical characteristics of a light emitting diode (LED).

The student builds a circuit to investigate how the current through an LED and the potential difference across it vary when the LED lights up.

Look at the circuit diagram.

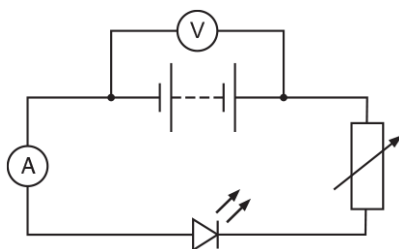

**i.** The student has made **two** errors connecting the circuit.

Identify the errors.


1

.....

2

.....

[2]

- ii. What is the purpose of the component  in the circuit?

[1]

(b). The student then connects the circuit correctly. He measures the current through the LED as 0.03 A when the potential difference across it is 3.0 V.

- i. Calculate the resistance of the LED.

Use the equation: potential difference = current  $\times$  resistance

Resistance = .....  $\Omega$  [3]

- ii. Calculate the charge which flows when this LED operates for 2.5 minutes.

Charge = ..... C [4]

- iii. Calculate the energy transferred when this LED operates for 2.5 minutes.

Use the equation: energy transferred = charge  $\times$  potential difference

Energy transferred = ..... J [2]




**10.** Calculate the charge when 200 J of energy is transferred with a potential difference of 40 V.


Use the equation: energy transferred = charge  $\times$  potential difference

Charge = ..... C [3]

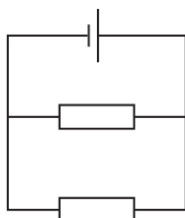**11 (a).** A student builds two electrical circuits. Each circuit uses identical cells and identical fixed resistors.



**A**

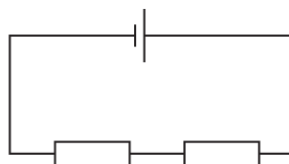

**B**

Explain why circuit **A** has a lower total resistance than circuit **B**.

-----

-----

----- [2]

**(b).** A student investigates the resistance of a filament lamp.

- i. Explain why the resistance of a filament lamp increases when current increases.

-----

-----

-----

----- [2]

- ii. Design a circuit diagram which could be used to investigate how the resistance of a filament lamp changes with current.

Use the circuit symbols below. Each symbol can be used once, more than once, or not at all.



[2]

- iii. Describe how the student would use the circuit you have drawn in (ii) to investigate how the resistance of a filament lamp changes with current.

-----

-----

-----

-----

-----

-----

[3]

12. Water can be heated using a 12 V heater.

A transformer is used to change a 120 V supply into 12 V.  
The current in the secondary coil is 9.0 A.

Calculate the current in the primary coil.

Use an equation from the data sheet.

Current = ..... A [2]

**END OF QUESTION PAPER**