
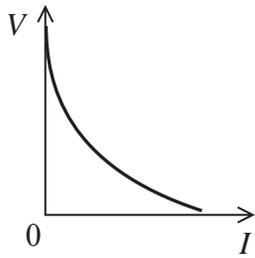


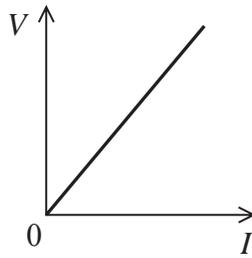
- 1 Which of the following graphs of potential difference  $V$  against current  $I$  correctly shows the behaviour of a filament lamp?




A



B

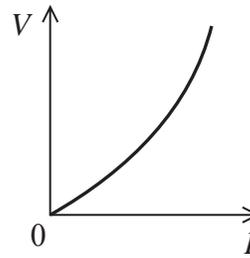

C

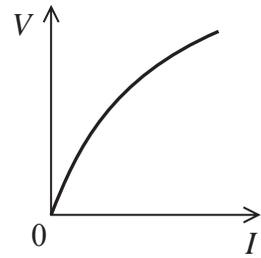

D

- A
- B
- C
- D

(Total for Question = 1 mark)

- 2 A rechargeable cell carries the marking 150 milliamp hours<sup>2</sup>  
What charge does this correspond to?

- A 9 C
- B 540 C
- C 9000 C
- D 540 000 C

(Total for Question = 1 mark)

3 The current in a filament lamp is 250 mA.

How much charge flows through the lamp in 3 minutes?

- A 0.75 C
- B 45 C
- C 750 C
- D 45 000 C

(Total for Question 1 mark)

4 A rechargeable cell stores a maximum energy of 4200 J. The cell has an e.m.f. of 1.5 V and after 2.0 hours use the cell is completely discharged.

Assuming the e.m.f. stays constant, the charge passing through the cell during this time is

- A 1400 C
- B 2800 C
- C 5600 C
- D 6300 C

(Total for Question = 1 mark)

5 An electric motor with potential difference  $V$  and current  $I$  lifts a mass  $m$  through a height  $h$  in time  $t$  at a steady speed  $v$ .

The efficiency of the motor is given by

- A  $\frac{1}{2}mv^2$   
 $VIt$
- B  $\frac{VI}{mg}$
- C  $\frac{VIt}{mv}$
- D  $\frac{mgh}{VIt}$

(Total for Question = 1 mark)

6 A current of 0.2 A flows through a lamp for 3 hours.

The total charge passing through the lamp in this time is

A 2160 C


B 600 C

C 36 C

D 0.6 C

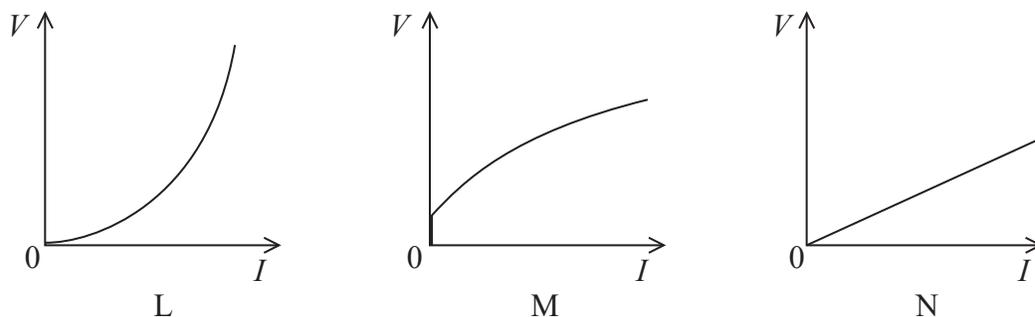**(Total for Question = 1 mark)**

7 The graphs show the variation of potential difference  $V$  with the current  $I$  for three components.







The three components are a metal wire at constant temperature, a filament lamp and a diode.

Which row of the table correctly identifies these graphs?

	<b>Metal wire at constant temperature</b>	<b>Filament lamp</b>	<b>Diode</b>
<input type="checkbox"/> <b>A</b>	L	M	N
<input type="checkbox"/> <b>B</b>	L	N	M
<input type="checkbox"/> <b>C</b>	N	M	L
<input type="checkbox"/> <b>D</b>	N	L	M

(Total for Question = 1 mark)

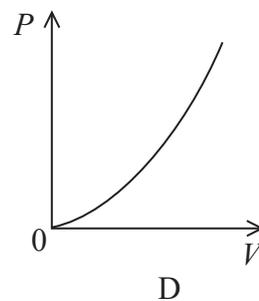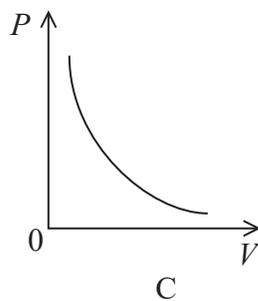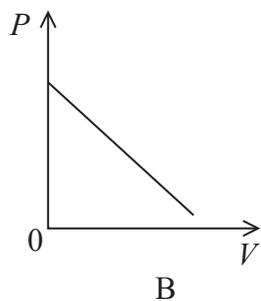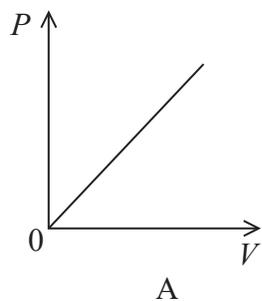8 The graphs show possible variations of power  $P$  with potential difference  $V$ .




Which graph is correct for a resistor that obeys Ohm's law?

- A
- B
- C
- D

(Total for Question = 1 mark)

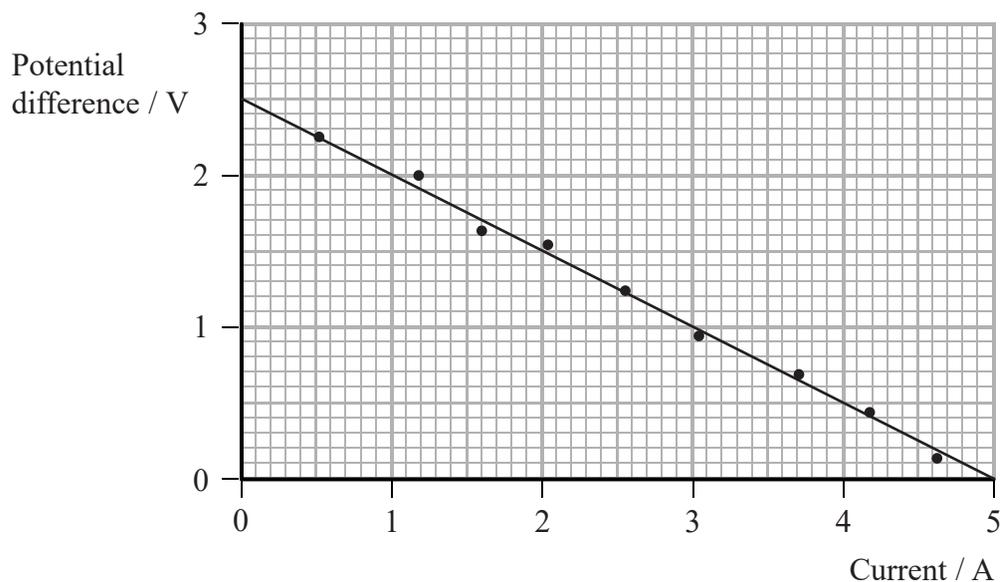- 9 A student wants to find the internal resistance of a cell. He plots a graph of the potential difference across the terminals of the cell against the current through the cell.



Which of the following quantities gives the internal resistance of the cell?


- A The area under the graph.
- B The intercept on the current axis.
- C The intercept on the potential difference axis.
- D The magnitude of the gradient.

(Total for Question = 1 mark)


10 The diagrams show connected wires that carry currents  $I_1$ ,  $I_2$ ,  $I_3$  and  $I_4$ .

The currents are related by the equation  $I_1 + I_2 = I_3 + I_4$

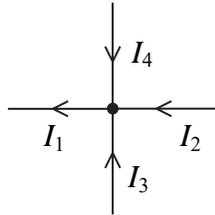
Identify the diagram that this equation applies to.




A

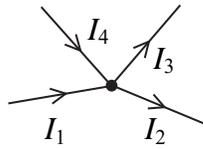

B

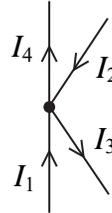

C

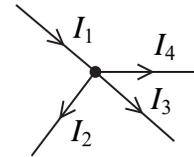

D

- A
- B
- C
- D


(Total for Question = 1 mark)

11 A 100 W lamp connected to the 230 V mains is replaced by a lamp which has twice the resistance. The power of the new lamp is

- A 25 W
- B 50 W
- C 200 W
- D 400 W

(Total for Question = 1 mark)

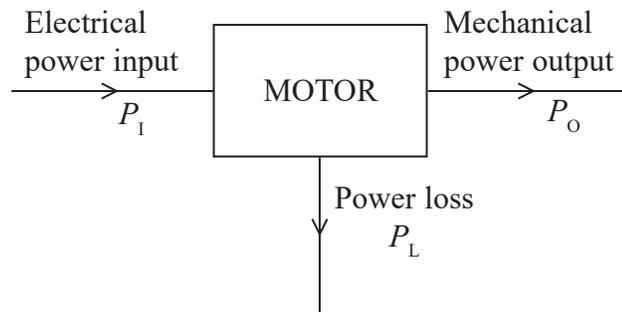12 Electrical power is transferred in a motor as shown.



What is the efficiency of the motor?

- A  $\frac{P_O + P_L}{P_I}$
- B  $\frac{P_I}{P_O}$
- C  $\frac{P_L}{P_I}$
- D  $\frac{P_O}{P_I}$

(Total for Question = 1 mark)

13 During a thunderstorm, a flash of lightning resulted in 600 000 C of charge flowing in a lightning conductor in a time of 40 ms. The current in the conductor was

- A  $1.5 \times 10^4$  A
- B  $2.4 \times 10^4$  A
- C  $1.5 \times 10^7$  A
- D  $2.4 \times 10^7$  A

(Total for Question = 1 mark)

14 The amount of electrical energy transferred when a charge of 8 mC moves through a potential difference of 12 V is

- A 1500 J
- B 96 J
- C  $9.6 \times 10^{-2}$  J
- D  $6.7 \times 10^{-4}$  J

(Total for Question = 1 mark)


15 A resistor is connected to a cell. An amount of charge  $Q$  passes through the resistor in a time  $t$ . During this time, the amount of chemical energy converted to electrical energy by the cell is  $E$ .

Select the row of the table which correctly gives the current in the resistor and the e.m.f. of the cell.

		Current	e.m.f.
<input type="checkbox"/>	A	$Q/t$	$EQ$
<input type="checkbox"/>	B	$Qt$	$EQ$
<input type="checkbox"/>	C	$Q/t$	$E/Q$
<input type="checkbox"/>	D	$Qt$	$E/Q$

(Total for Question = 1 mark)

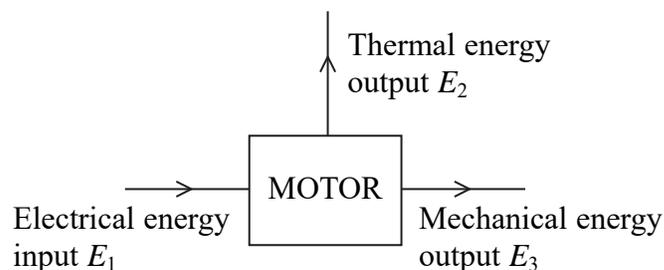16 The diagram shows the energy transfer for an electric motor.



The efficiency of the motor is

- A  $\frac{E_1}{E_2 + E_3}$
- B  $\frac{E_1}{E_2}$
- C  $\frac{E_3}{E_1}$
- D  $\frac{E_2 + E_3}{E_1}$





(Total for Question = 1 mark)

17 A child's toy is operated by a small motor. The potential difference across the motor is 6.0 V and the current in it is 0.20 A. The energy used by the motor in 120 s is

- A 2.40 J
- B 60.0 J
- C 144 J
- D 3600 J

(Total for Question = 1 mark)

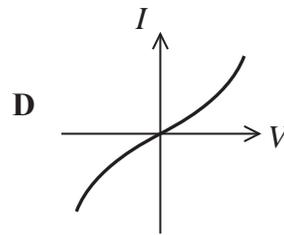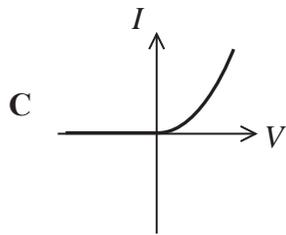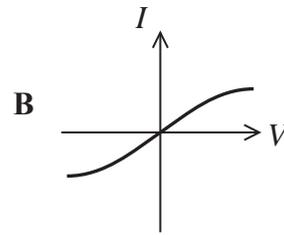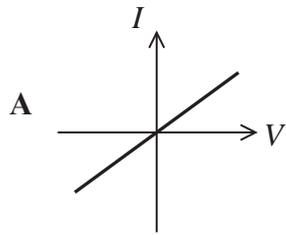18 Which of the following current-potential difference ( $I$ - $V$ ) graphs correctly shows the behaviour of a diode?



A





B

C

D

(Total for Question = 1 mark)

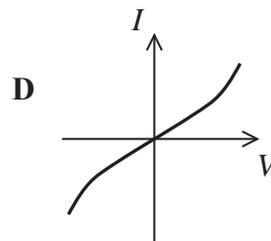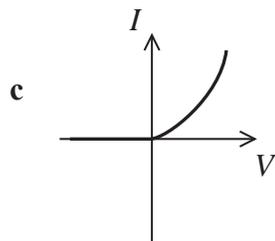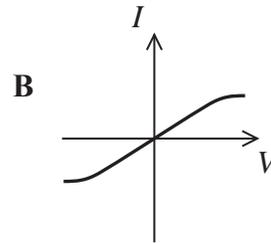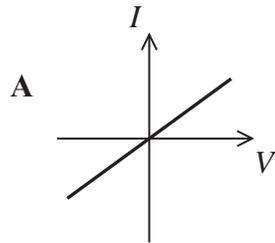19 Which of the following current – potential difference ( $I$ – $V$ ) graphs shows the correct behaviour for a filament bulb?



A

B

c

D

(total for Question = 1 mark)

20 Which of the following SI units is equivalent to the volt?

A ampere per ohm

B coulomb per second

C joule per coulomb

D joule per second

(Total for Question = 1 mark)