

Question Number	Answer	Mark
1(a)	Charges (1) Movement of electrons from one plate to the other OR one plate becomes + the other - OR until pd across C equals $V_{\text{supply}}$ (1)	2
1(b)(i)	Use of $Q = It$ (both 0.74 and 0.1/0.2) (1) Recognition of milli and $\Delta t = 0.1$ (1)  Eg $Q = 0.74 \times 10^{-3} \times 0.1 = 74 \times 10^{-6} \text{ C}$	2
1(b)(ii)	Use of $V = Q/C$ (1) Explains unit conversion (1)  Eg $V = 278 \times 10^{-6} / 100 \times 10^{-6} = 2.78$ [accept $\mu/\mu$ ]	2
1(c)(i)	Recall of $RC$ (1) Answer = 0.3 (s) (1) Eg $T = 3000 \times 0.0001$  <b>plus either</b> 1/e or 37% of initial (1) =0.23 - 0.27 (s) (1)  <b>or</b> sub in formula $I = I_0 e^{-t/RC}$ (1) = 0.23 - 0.27 (s) (1)  <b>or</b> Initial Tangent drawn (1)	
	Time constant = 0.2-0.3 (s) (1)	4
1(c)(ii)	Plot $\ln I / \log I$ (1) Against $t$ (1) (dependent on first mark) or Gradients of graph (1) Against $I$ (1) (dependent on first mark)  should be straight line (1) (dependent on previous 2)	3
	<b>Total for question</b>	<b>13</b>

Question Number	Answer	Mark
<b>2(a)</b>	The capacitor stores charge <b>Or</b> capacitor charges from the supply The idea that the capacitor doesn't fully discharge before being recharged.	(1) (1) <b>2</b>
<b>2(b)(i)</b>	$(6.4 + 4.4)/2 = 5.4 \text{ V}$	(1) <b>1</b>
<b>2(b)(ii)</b>	Use of $V = IR$ Average $I = 5.4 \text{ V}/(2.2 \times 10^3 \Omega) = 2.5 \times 10^{-3} \text{ A}$ ecf value from (b)(i)	(1) (1) <b>2</b>
<b>2(b)(iii)</b>	Time = 17 ms or 17.5 ms	(1) <b>1</b>
<b>2(b)(iv)</b>	Use of $Q = It$ Use of $C = Q/V$ Use of $\Delta V = 2.0 \text{ V}$ $C = 21 \mu\text{F}$ (ecf values of $I$ and $t$ from above)  <u>Example of calculation</u> $Q = 2.5 \times 10^{-3} \text{ A} \times 17 \times 10^{-3} \text{ s} = 4.25 \times 10^{-5} \text{ C}$ $C = 4.25 \times 10^{-5} \text{ C} / 2.0 \text{ V}$ $C = 21 \mu\text{F}$	(1) (1) (1) (1) <b>4</b>
<b>2(c)</b>	Uses a larger capacitance  Because a larger time constant is needed <b>Or</b> stores more charge <b>Or</b> less $\Delta V \rightarrow \Delta Q/C$	(1)   (1) <b>2</b>
<b>Total for question 17</b>		<b>12</b>

