

Question		Answer	Marks	Guidance	
1	a	p.d./voltage (across component) divided by current (in it)	B1	accept V/I with V and I defined; per (unit) current, etc	
	b	i	R = $\rho l/A$ $= 1.7 \times 10^{-8} \times 20 \times d/4d^2 = 1.7 \times 10^{-8} \times 5/3.8 \times 10^{-10}$ $= 220 \text{ } (\Omega)$	C1 C1 A1	allow $A = 4\pi r^2 = 4.5 \times 10^{-19}$ giving $285 \text{ } \Omega$ accept 220 to $230 \text{ } \Omega$
		ii	$n = 1/d^3 = (1.8 \times 10^{28})$	A1	accept alternatives, e.g. 80/volume
		iii	$I = nAev$ $= 1.8 \times 10^{28} \times 4 \times (3.8 \times 10^{-10})^2 \times 1.6 \times 10^{-19} \times 1.9 \times 10^{-5}$ $= 3.2 \times 10^{-14} \text{ (A)}$	C1 A1	1 mark for substitution into formula, ecf n, A values accept 3.16 and 3.5 (using $n = 2 \times 10^{28}$) accept 2.48 and 2.76 (for $285 \text{ } \Omega$)
		iv	$P = I^2R$ $= (3.2 \times 10^{-14})^2 \times 200 \times 10^9$ $= 2.0 \times 10^{-16} \text{ (W)}$	C1 C1 A1	ecf b(i) & (iii) accept 1 SF as estimate; can obtain 1.2 to 2.8 using all values possible in (iii)
	c	electron moves at drift velocity signal travels at/close to the speed of light	B1 B1	accept answers explaining idea of drift velocity	
Total			12		

Question		Expected Answers	M	Additional Guidance
2				
	a	current moves from + to – (of battery in circuit) and electrons move from – to +	B1	
	b	$C s^{-1} V \Omega^{-1}$	B1 B1	2 correct 2 marks; 1 correct 1 mark, withhold a mark for each additional answer given
	c	i	B1	accept wires are in <u>series</u> or current is the same (at every point) in a <u>series</u> circuit/AW not current in = current out
		ii1	B1 A1	accept $R \propto l$ and $R \propto 1/A$ or similar method/argument must be convincing accept $3/2 \times 12$ but not $3 \times 2 \times 12$
		ii2	C1 A1	accept R_s in series ecf (c)(ii)1
		iii	B1 B1	allow $v \propto 1/A$ accept $4 \times 10^{-5} (m s^{-1})$ no SF error
		Total question 1	10	

Question		Expected Answers	Marks	Additional Guidance
3	(a)	$E = I(R + r)$	B1	
	(b)	(i) 1 2 0.80 Ω 6.4 V	B1 B1	
		(ii) (sum of) e.m.f.s = sum /total of p.d.s/sum of voltages (in a loop)	B1	
		(iii) $6.4 = 0.80I$ $I = 8.0 \text{ A}$	C1 A1	can be 2 ecf from (b)(i), eg $21.6/0.8 = 27 \text{ A}$ (1 ecf) or $21.8/0.68 = 31.8 \text{ A}$ (2 ecf)
	(c)	(i) $Q = It = 2.5 \times 6 \times 60 \times 60$ $= 54000 \text{ (C)}$	C1 A1	allow 1 mark if forgets one or two 60's giving 900 C or 15 C
		(ii) energy = $QE = 54000 \times 14$ $= 756000 \text{ (J)}$	C1 A1	allow (use of 12 V gives) 648000 J for 1 mark
		(iii) energy loss = $I^2Rt = VIt = 2 \times 2.5 \times 6.0 \times 60 \times 60 = 108000 \text{ J}$ percentage = $(108000/756000) \times 100 = 14\%$	C1 A1	accept $Q\Delta V = 54000 \times 2.0 = 108000 \text{ J}$ accept $Q\Delta V/QE = 2.0/14.0 = 14\%$ not $756000/54000 = 14\%$
		Total question 2	12	

Question			Expected Answers	M	Additional Guidance
4	a	i	ions	B1	
		ii	<u>positive</u> ions	B1	allow <u>positive</u> charges / cations
		iii	electrons	B1	
	b	i	the battery has an internal resistance/AW some of the emf is across the (internal) resistance (leaving a smaller p.d. across motor)	B1 B1	accept connecting leads have resistance accept $V = E - Ir$ or 'lost volts'/p.d. across r
		ii	use $E = V + Ir$ giving $12 = 8 + 40r$ $r = (12 - 8)/40$ or $4/40$ $= 0.10 \Omega$	C1 M1 M1 A0	accept reverse solution, $0.10 \Omega \rightarrow 8 \text{ V} \rightarrow 12 \text{ V}$ substitution and or solution showing working
		iii	$Q = It = 40 \times 1.2$ $I = 48 \text{ (C)}$	C1 A1	
	c	i	The current heats the filament The resistance/resistivity (of the metal filament) increases (with temperature).	B1 B1	no mention of temperature increase or heating scores zero
		ii	4.5 to 8 A in <u>each (parallel) arm</u> or 9 to 16 A for both together needs to be great enough to cover initial surge/current or use antisurge fuses	B1 B1	no mark if fuse value outside range
		iii	e.g. the starter motor draws 40 A so would need a bigger fuse than headlamp circuit so need different fuses for different situations or if battery used for starter motor with lights on will need too large a fuse – damage occurs before fuse blows/AW	B1	accept headlamp circuit damaged before fuse blows if 40 A fuse only used or fuse blows in starter circuit if 10 A used, etc.
Total question 2				15	