

Question		Expected Answers	Marks	Additional Guidance
<b>1</b>				
	<b>a</b>	<b>i</b>	$E = (Pt) = 36 \times 3600$ $= 1.3 \times 10^5 \text{ (J)}$	C1 A1 <b>allow</b> $I = 3 \text{ A}$ and $E = VIt$ , etc. <b>accept</b> 129600 (J)
		<b>ii</b>	$Q = E/V = 1.3 \times 10^5/12$ <b>or</b> $Q = It = 3 \times 3600$ $= 1.1 \times 10^4$ unit: C	C1 A1 B1 <b>ecf (a)(i)</b> <b>accept</b> $1.08 \times 10^4$ <b>allow</b> A s <b>not</b> $\text{J V}^{-1}$
		<b>iii</b>	$Q/e = 1.1 \times 10^4/1.6 \times 10^{-19}$ $= 6.9 \times 10^{22}$	C1 A1 <b>ecf (a)(ii)</b> <b>accept</b> 6.75 or $6.8 \times 10^{22}$ using 10800
	<b>b</b>	<b>i</b>	the average displacement/distance travelled of the electrons <u>along the wire</u> per second; (over time/on average) they move slowly in one direction through the metal/Cu lattice (when there is a p.d. across the wire); (because) they collide constantly/in a short distance with the lattice/AW	B1  B1 B1 no mark for quoting formula <b>allow</b> in one second  <b>max 2 marks</b> from 3 marking points
		<b>ii</b>	select $I = nAev$ ( $= 3.0 \text{ A}$ ) $v = 3.0/8.0 \times 10^{28} \times 1.1 \times 10^{-7} \times 1.6 \times 10^{-19}$ $= 2.1 \times 10^{-3} \text{ (m s}^{-1}\text{)}$	C1 C1 A1 1 mark for correct formula 1 mark for correct substitutions into formula 1 mark for correct answer to 2 or more SF
			<b>Total question 1</b>	<b>12</b>

Question			Answer	M	Guidance
<b>2</b>					
	<b>a</b>	<b>i</b>	$Q = It = 0.45 \times 4.67 \times 60 \times 60$ $= 7600$ C or As	C1 A1 B1	<b>accept</b> 7560 or 7570
		<b>ii</b> <b>1,2</b>	<b>1</b> positive; <b>2</b> clockwise  energy must be transferred to the cell <b>or</b> current in opposite direction transfers energy from the cell to the circuit/AW	M1  A1	positive plus correct direction of arrow for first mark; do not penalise if arrow not labelled I. <b>allow</b> (conventional) current is from positive to negative ; <b>or</b> electron flow from – to + [but current must be clockwise in <b>1</b> ]
		<b>3</b>	$V_{XY} = 1.5 + 0.45 \times 0.90$ $V_{XY} = 1.9 \text{ (V)}$	C1 A1	<b>accept</b> 1.905 or 1.91
		<b>4</b>	$P = VI = 0.45 \times 1.5$ $P = 0.675 \text{ (J s}^{-1}\text{)}$	C1 A1	<b>allow</b> QV/t with <b>ecf a(i)</b> if necessary (11340/16800) <b>allow</b> 0.7 as final line if 0.675 appears above
	<b>b</b>		<b>1.</b> cell across variable resistor R ammeter in series and voltmeter in parallel across R or cell <b>2.</b> Take (set of) readings of V and I for different positions/values of the variable resistor <b>3.</b> plot a graph of V against I <b>4.</b> (find) y-intercept = E <b>5.</b> (find) the gradient of the V against I graph which equals the internal resistance in magnitude <b>or 4 or 5</b> take one pair of values of V, I and substitute into equation $E = V + Ir$ to find r or E	B1  B1 B1 B1  B1	QWC last marking point needed for full marks  <b>allow</b> use (digital) voltmeter across <u>unloaded</u> cell to find E; add R and find one value of V and I; then use equation to find r (points 2 to 5) <b>ignore</b> sign of gradient in determining r <b>allow</b> for no graph plot, using 2 pairs of values of V and I substituted into equation allows r and E to be found.(points 2 to 5)
	<b>c</b>	<b>i</b>	4 x 1.5 V cells gives 6.0 V with r of 3.6 $\Omega$ so current is $6.0 / (3.6 + 18) = 0.28 \text{ A}$ requires (2 W/6 V = ) 0.33 A to light normally or power delivered = $(0.28^2 \times 18 \text{ or } 5.0 \times 0.28) = 1.4 \text{ W}$ <b>alt:</b> use 0.33 A & 6 V to show need emf of 7.2 V (1.8 V per cell)	B1 B1 B1	<b>allow</b> AW such as: 6 V but total R now 21.6 $\Omega$ ; 6 V across 21.6 $\Omega$ gives 5 V across 18 $\Omega$ ; requires 6 V to light normally <b>allow</b> $P = 1.(6)7 \text{ W}$ for 2 marks; only give the third mark if P labelled as power delivered by cell
		<b>ii</b>	$1.5 n = 0.33 (18 + 0.9 n) \text{ or } 1.5n = 6 + 0.3n$ so $3.6 n = 18 \text{ or } 1.2n = 6$ giving $n = 5$	M1 A1	<b>alt:</b> lamp needs $V = 6\text{V}$ and $I = 0.33 \text{ A}$ terminal p.d per cell is $1.5 = V + 0.9 \times 0.33$ giving $V = 1.2 \text{ V}$ so $n = 6/1.2 = 5$ <b>allow</b> trial and error method but working must be shown to score any marks
			<b>Total question 3</b>	<b>19</b>	

Question			Expected Answers	M	Additional Guidance
<b>3</b>					
	<b>a</b>	<b>i</b>	(sum of/total) current into a junction equals the (sum of/total) current out conservation of charge	B1 B1	total vector sum of currents is zero
		<b>ii</b>	(sum of) e.m.f.s = (sum /total of) p.d.s/sum of voltages in/around a (closed) loop (in a circuit) energy is conserved	B1 B1	
	<b>b</b>		a photon is absorbed by an electron (in a metal surface); causing electron to be emitted (from surface). Energy is conserved (in the interaction).	B1 B1 B1	<b>not hits</b> QWC mark
			Only photons with energy/frequency above the work function energy/threshold frequency will cause emission Reference to Einstein's photoelectric energy equation (energy of photon) = (work function of metal) + (maximum possible kinetic energy of emitted electron) work function energy is the <u>minimum</u> energy to release an electron from the surface Number of electrons emitted also depends on light intensity Emission is instantaneous	B1 B2 B1 B1 B1	3 marks from 6 marking points in symbols only scores 1 mark out of 2, i.e. selects from formula sheet
			<b>Total question 5</b>	<b>10</b>	

Question			Answer	Marks	Guidance
4	(a)	(i)	<u>sum of/total</u> current into a junction equals the <u>sum of/total</u> current out conservation of charge	B1 B1	total vector sum of currents is zero <b>allow</b> ' <u>point in a circuit</u> ' for 'junction'
		(ii)	(sum of) e.m.f.s = <u>sum /total</u> of p.d.s/sum of voltages in/around a (closed) loop (in a circuit) energy is conserved	B1 B1	<b>allow</b> 'in a (closed) circuit' in place of 'loop'
	(b)	(i)	current in $750 \Omega = 0.020 \text{ A}$	A1	<b>allow</b> 20 mA or 0.02 A
		(ii)	V across $750 \Omega = 0.02 \times 750 = 15 \text{ V}$	A1	<b>ecf b(i)</b>
		(iii)	$R_1 = (45 - 15)/0.03 = 1000 \Omega$ $R_2 = 15/0.01 = 1500 \Omega$	A1 A1	<b>ecf b(ii)</b>
	(c)	(i)	correct symbol connected in circuit	B1	2 arrows pointing towards the resistor at about $45^\circ$ with or without a circle; arrows outside circle if drawn
A A A		(ii)	<u>total R</u> falls so I <u>in circuit/in</u> $R_1$ increases so V across $R_1$ increases <u>and</u> V across $750 \Omega$ falls	B1 M1 A1	<b>accept</b> sum of R's in parallel falls $R_1$ is fixed so V across $R_1$ increases so V across R's in parallel falls (so V across $750 \Omega$ falls) <b>or</b> correct potential divider argument
		(iii)	in series with LDR ammeter (A)  50 mA	M1 A1 B1	<b>allow</b> voltmeter in parallel with $R_1$ (30 – 50 V) <b>allow</b> multimeter connected as A (series) or V (parallel) and a correct unit for range given <b>allow</b> 20 to 100 mA; or 15 to 50 V
			<b>Total</b>	<b>15</b>	