Question		on	Expected Answers		Additional Guidance
1					
	а	i	no current/no light/does not conduct until V is greater than 1.5 V	B1	allow 1.4 to 1.6 V (QWC mark)
			brightness/intensity of LED increases with current/voltage above 1.5 V	B1	(alternative QWC mark)
			above 1.8 V current rises almost linearly with increase in p.d./AW	B1	
			the LED does not obey Ohm's law	M1	
			as I is not proportional to V/AW	A1	
			below 1.5 V, LED acts as an infinite R/ very high R/acts as open switch	B1	max 5 marks which must include at least
			above 1.5 V, LED resistance decreases (with increasing current/voltage)	B1	one of the first 2 marking points
		ii 1	infinite resistance	B1	
		2	$I = 23.0 \pm 1.0 \text{ (mA)}$	C1	
			$R = 1.9 \times 10^{3} / (23 \pm 1) = 83 \pm 4 \Omega$	A1	apply POT error for 0.083 Ω
	b		LED symbol with correct orientation	B1	diode symbol + circle + at least one arrow
			resistor (need not be labelled) and ammeter in series with it	B1	pointing away
			voltmeter in parallel across LED only	B1	
	С		the resistor limits the <u>current</u> in the circuit (when the LED conducts)	B1	
			otherwise it could overheat/burn out/be damaged/AW	B1	
	d		in fig 4.3 the voltage range is from zero to maximum possible	B1	allow 6.0 V
			in fig. 4.2 the resistance variation is small/AW	B1	accept the LED is part of a potential divider
			(so) in fig. 4.2 voltage variation across LED is small	B1	accept only at the top end of the range/AW
			Total question 4	16	

Question		on	Answer		Guidance	
2	а	i	ammeter in series voltmeter in parallel with LED	B1	both correct to score 1 mark	
		ii	(at 20 mA) V_{led} = 4.0 V V _R = 0.020 x 100 = 2.0 V so p.d. = 6.0 V	B1 C1 A1	allow R _{led} = (4.0/ 0.02) = 200 Ω p.d. = 0.020 (200 + 100) allow answer to 1 SF	
	b	i	energy in eV = $4.1 \times 10^{-19}/1.6 \times 10^{-19} = 2.6$ (eV)	B1	expect 2.56 eV	
		ii	LED strikes at 2.6 V/ only conducts above 2.6 V an electron must pass through a p.d. of 2.6 V to lose energy as a photon of blue light/AW.	M1 A1		
	С	i	$n = I/e = 0.02/1.6 \times 10^{-19}$ = 1.3 x 10 ¹⁷	C1 A1	expect 1.25 x 10 ¹⁷	
		ii	energy/s = 1.25 x 10 ¹⁷ x 4.1 x 10 ⁻¹⁹ or 2.6 V x 0.020 A = 0.051 to 0.053 (J s ⁻¹)	C1 A1	ecf (c)(i); NOT 4.0 x 0.020 answer is 0.053 using 1.3 x 10 ¹⁷	
		iii	efficiency = 0.052/(4.0 x 20 x 10 ⁻³) = 0.64	C1 A1	ecf (c)(ii) accept V _{strike} /V _{operate} = 2.6/4.0 or any other correct (P or W out)/ (P or W in) calculation accept 64 %	
	d		shape similar to the curve drawn leaving x-axis at close to 2.0 V and passing through (3.4, 20)	B1 B1	Within half a square	
			Total	15		

Question		ion	Answer		Marks	Guidance	
3	(a)	(i)	sum of/total current into a junction equals th current out conservation of charge	ne <u>sum of/total</u>	B1 B1	total vector sum of currents is zero allow 'point in a circuit' for 'junction'	
		(ii)	(sum of) e.m.f.s = <u>sum /total</u> of p.d.s/sum of a (closed) loop (in a circuit) energy is conserved	f voltages in/around	B1 B1	allow 'in a (closed) circuit' in place of 'loop'	
	(b)	(current in 750 Ω = 0.020 A		A1	allow 20 mA or 0.02 A	
		(ii)	V across 750 Ω = 0.02 x 750 = 15 V		A1	ecf b(i)	
		(iii)	$R_1 = (45 - 15)/0.03 = 1000 \Omega$ $R_2 = 15/0.01 = 1500 \Omega$		A1 A1	ecf b(ii)	
	(c)	(correct symbol connected in circuit		B1	2 arrows pointing towards the resistor at about 45 ⁰ with or without a circle; arrows outside circle if drawn	
A A A		(ii)			B1 M1 A1	accept sum of R's in parallel falls R_1 is fixed so V across R_1 increases so V across R's in parallel falls (so V across 750 Ω falls) or correct potential divider argument	
		(iii)	in series with LDR i ammeter (A) 50 mA 2	n parallel with LDR voltmeter (V) 20 V	M1 A1 B1	allow voltmeter in parallel with $R_1 (30 - 50 V)$ allow multimeter connected as A (series) or V (parallel) and a correct unit for range given allow 20 to 100 mA; or 15 to 50 V	
				Total	15		