

Question		Expected Answers	Marks	Additional Guidance
1	a	Capacitance = charge per (unit) potential difference	B1	Allow: capacitance = charge / potential difference, charge/pd, charge/voltage but not charge / volt, coulomb /pd (no mixture of quantities and units. Allow 'over' instead of per
	b	(i) $Q = CV = 4.5 \mu \times 6.3 = 28.(35) (\mu C)$	B1	Allow: 28 (≥ 2 sf)
		(ii) $E = \frac{1}{2} CV^2 = 0.5 \times 4.5 \times \mu \times (6.3)^2$ $= 8.9(3) \times 10^{-5} (J) / 89.3 \mu(J)$	C1 A1	Allow use of $E = \frac{1}{2} QV$ and the Q value from (b)(i) $Q=28 E= 8.82$ and $Q=28.4 E=8.946$ Allow ecf from (b)(i) penalise power of ten error (-1)
	c	(i) Electrons / they move in an anticlockwise direction Charge on plates decreases / electrons neutralise positive charge p.d. decreases <u>exponentially</u>	B1 B1 B1	Alternatives for anticlockwise: from / lower plate around the circuit, from / lower plate through the resistor to top plate implied Capacitor discharges / loses charge
		(ii) (dissipated as heat) in the resistor / wires	B1	
	d	(i) Total capacitance = $1.5 + 4.5 = 6(.0) (\mu F)$	A1	Allow one SF
		(ii) Original charge on $4.5 \mu F$ capacitor is conserved ($28.35 \mu C$) $V = (28.35 \mu) / (1.5 + 4.5) \mu = 4.7 (V)$	C1 A1	ecf from (b)(i) and (d)(i)
		Total	[11]	

Question			answer	Marks	Guidance
2	(a)	(i)	Any <u>two</u> from: Correct direction of movement of electrons Electrons deposited on Y / removed from X An equal number of electrons removed and deposited on plates (AW)	B1 × 2	
		(ii)1	$Q = 40 \times 10^{-6} \times 100 (= 4.0 \times 10^{-3} \text{ C})$ $4.0 \times 10^{-3} = 1.6 \times C$ $C = 2.5 \times 10^{-3} \text{ (F)}$	C1 C1 A1	Allow: 2 marks for $2.5 \times 10^n \text{ (F)}$, where $n \neq -3$ (POT error)
		(ii)2	Graph starts at <u>origin</u> and has positive gradient A straight line graph that passes between 1-2 V at 100 s	M1 A1	
	(b)	(i)	$CR = 4.7 \times 10^{-6} \times 220 (= 1.03 \times 10^{-3} \text{ s})$ $4.00 = 6.00e^{-\frac{t}{1.03 \times 10^{-3}}}$ $t = -\ln(4.00/6.00) \times 1.03 \times 10^{-3}$ time = $4.2 \times 10^{-4} \text{ (s)}$	C1 C1 A1	Note: Answer to 3 sf is $4.19 \times 10^{-4} \text{ (s)}$ Allow: 2 marks for $t = -\lg(4.00/6.00) \times 1.03 \times 10^{-3} = 1.8 \times 10^{-4} \text{ s}$
		(ii)	speed = $\frac{0.100}{4.2 \times 10^{-4}}$ speed = $240 \text{ (m s}^{-1}\text{)}$	B1	Possible ecf from (b)(i)
Total				11	

Question		Answers	Marks	Guidance
3	(a)	capacitance = charge/p.d. or capacitance = charge per (unit) p.d.	B1	Allow: voltage instead of p.d. Note: Do not allow mixture of quantity and unit, e.g. 'charge per (unit) volt'
	(b) (i)	$C_{\text{parallel}} = 240 \text{ } (\mu\text{F})$ $C_T = (240 \times 120)/(240 + 120)$ or $C_T = (240^{-1} + 120^{-1})^{-1}$ total capacitance = 80 (μF)	C1 C1 A0	Allow :1 mark if C_T is not the subject, e.g: $\frac{1}{C_T} = \frac{1}{240} + \frac{1}{120}$
	(ii)	$E = \frac{1}{2} V^2 C$ $E = \frac{1}{2} \times 6.0^2 \times 80 \times 10^{-6}$ energy = 1.4×10^{-3} (J) or 1.44×10^{-3} (J)	C1 A1	Possible ecf Allow: 1 mark for an answer 1.44×10^n ($n \neq -3$)
	(iii)	$6.0/e = 2.2$ (V) (as on graph) Or $6.0 \times 0.37 = 2.2$ (V) (as on graph) Or At 20 (s), $V = 2.2$ (V), $2.2/6.0 = 0.37$ (or e^{-1})	B1	Allow: Graph reading within ± 0.2 V
	(iii)	$CR = 20$ $R = \frac{20}{80 \times 10^{-6}}$ $R = 2.5 \times 10^5$ (Ω)	C1 A1	Allow: Follow through with CR value from (iii)1
Total			8	

Question		Expected Answer	Mark	Additional Guidance
4	(a)	coulomb <u>per</u> volt	B1	Allow: 1 F = 1 <u>CV⁻¹</u>
	(b)	(i) <u>Electrons</u> flow 'clockwise' / negative to positive These are deposited on (plate) A (and hence becomes negatively charged) or These are removed from (plate) B (and hence become positively charged)	B1 B1	Not: A becomes negative / B becomes positive
		(ii) $Q = C \times V = 5.4 \times 10^{-9} \times 12$ charge = 6.48×10^{-8} (C)	B1	
		(ii) energy = $\frac{1}{2} V^2 C = \frac{1}{2} \times 12^2 \times 5.4 \times 10^{-9}$ energy = 3.89×10^{-7} (J)	B1	Possible ecf if Q used from (ii)1
	(c)	(i) $R = \frac{12}{3.24 \times 10^{-6}}$ resistance = 3.7×10^6 (Ω)	M1 A0	Allow: 'R = 12/3.24 μ ' (= 3.7 M Ω)
		(ii) time constant = CR = $5.4 \times 10^{-9} \times 3.7 \times 10^6$ or 0.02 (s) $I = I_0 e^{-t/CR} = 3.24 \times e^{-(0.080/0.020)}$ current = 0.059 (μ A)	C1 A1	Allow: ecf for time constant Allow: 1 mark for 5.9×10^{-11}
	(d)	(Total) resistance of circuit <u>halved</u> / time constant is <u>halved</u> Rate of discharge is <u>doubled</u> / (initial) current is <u>doubled</u>	B1 B1	
		Total	10	